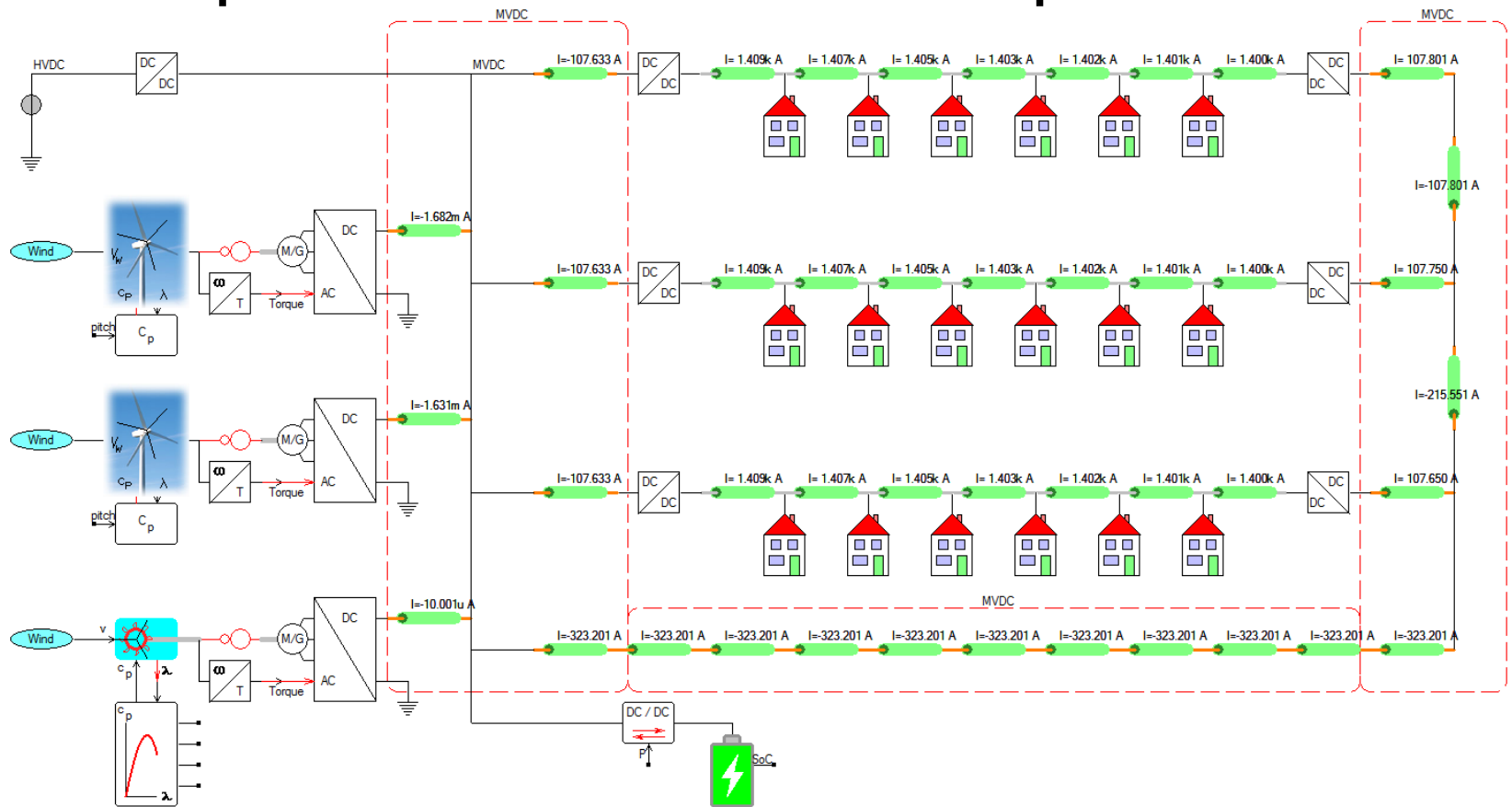


Droop Control

Peter van Duijsen


HHS / Simulation Research

www.caspoc.com/news/workshops/dctrees




Contents

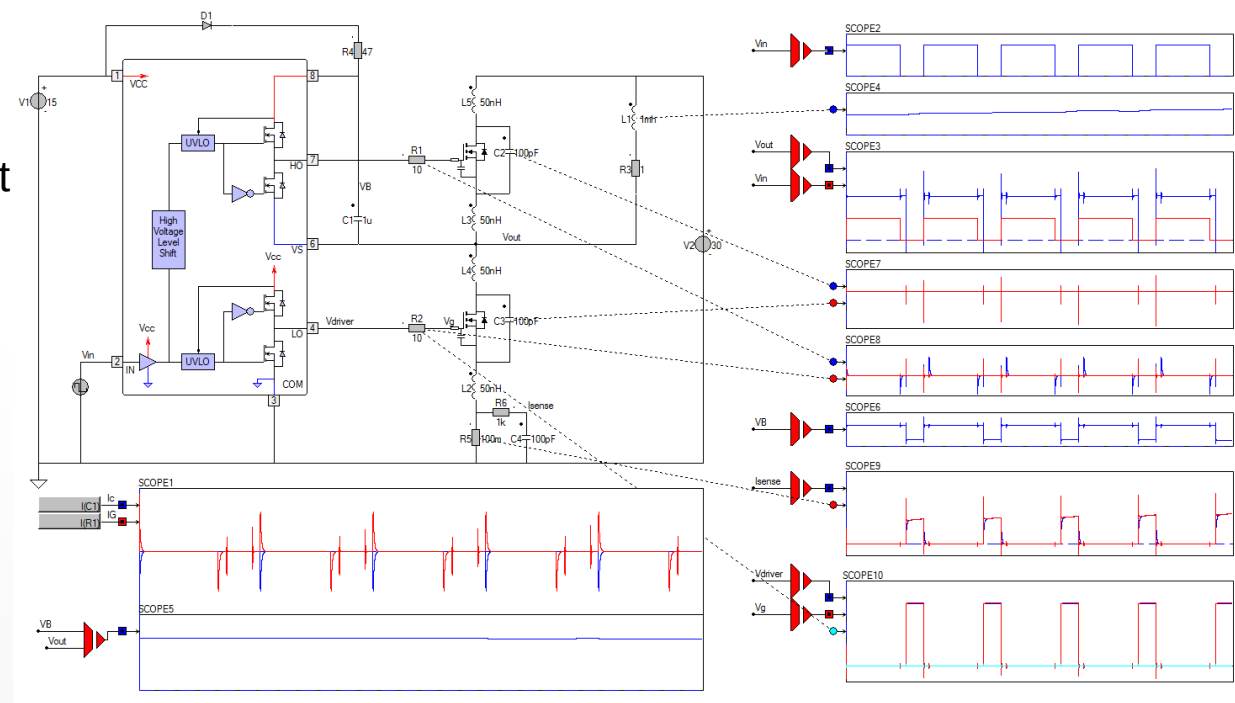- Introduction, what is droop control?
- Part I Methods
 - Introduction
 - Configuration DC grid
 - 9volt battery example
 - Power Electronics
- Part II Components
 - Grid
 - Solar
 - Battery
- Part III Congestion Management
 - 9 volt Battery example
 - 380 volt example
 - Droop example
- Conclusion






Introduction

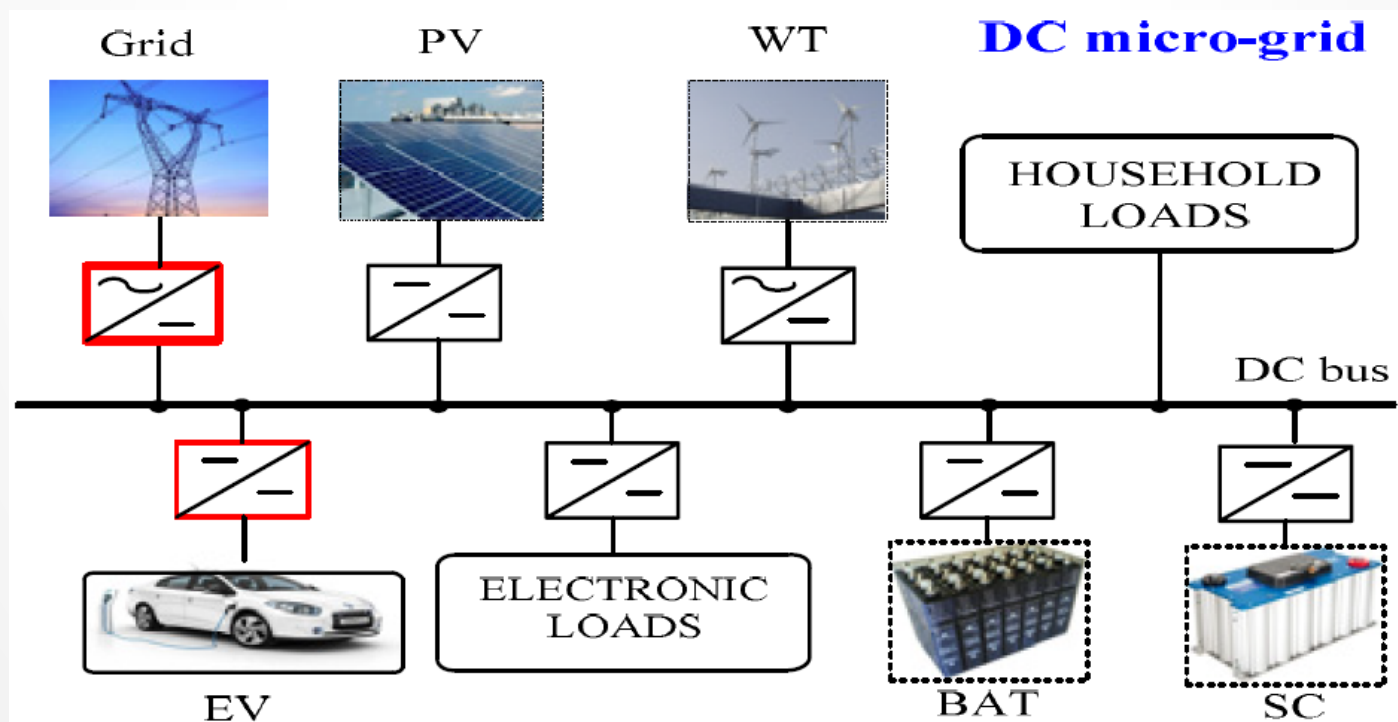- What is droop control?
- Why do we need it?
- Is it easy to implement?



Configuration

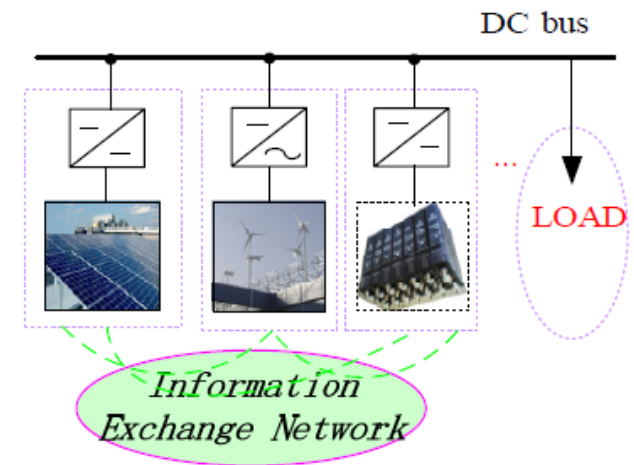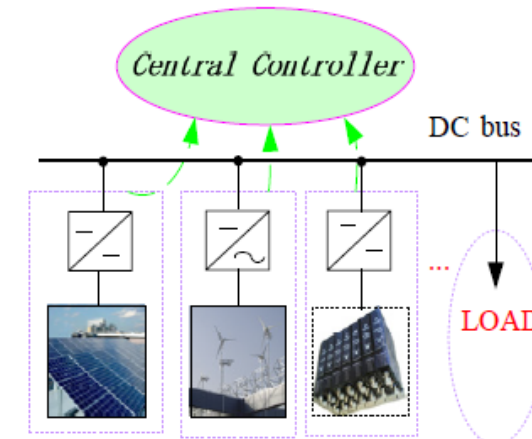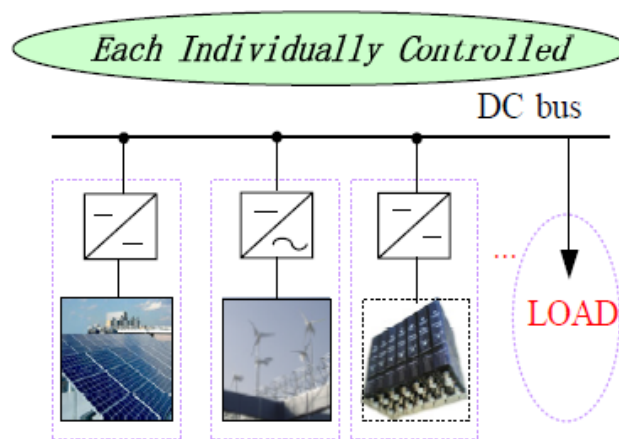- Decentralized control
- Centralized control
- Distributed control




(a) Decentralized control

(b) Centralized control


(c) Distributed control

Connecting everything just like that?

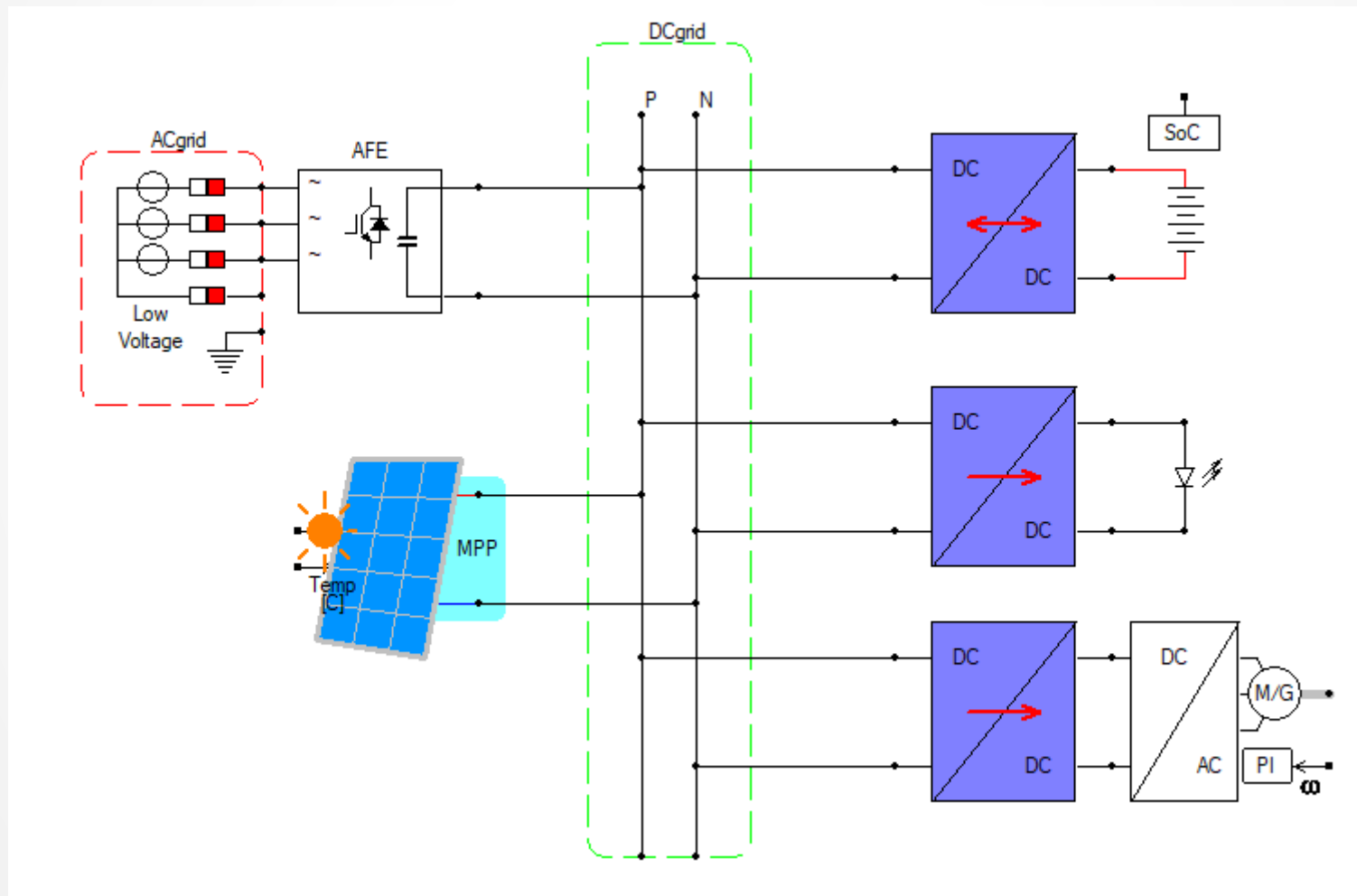


9volt battery example

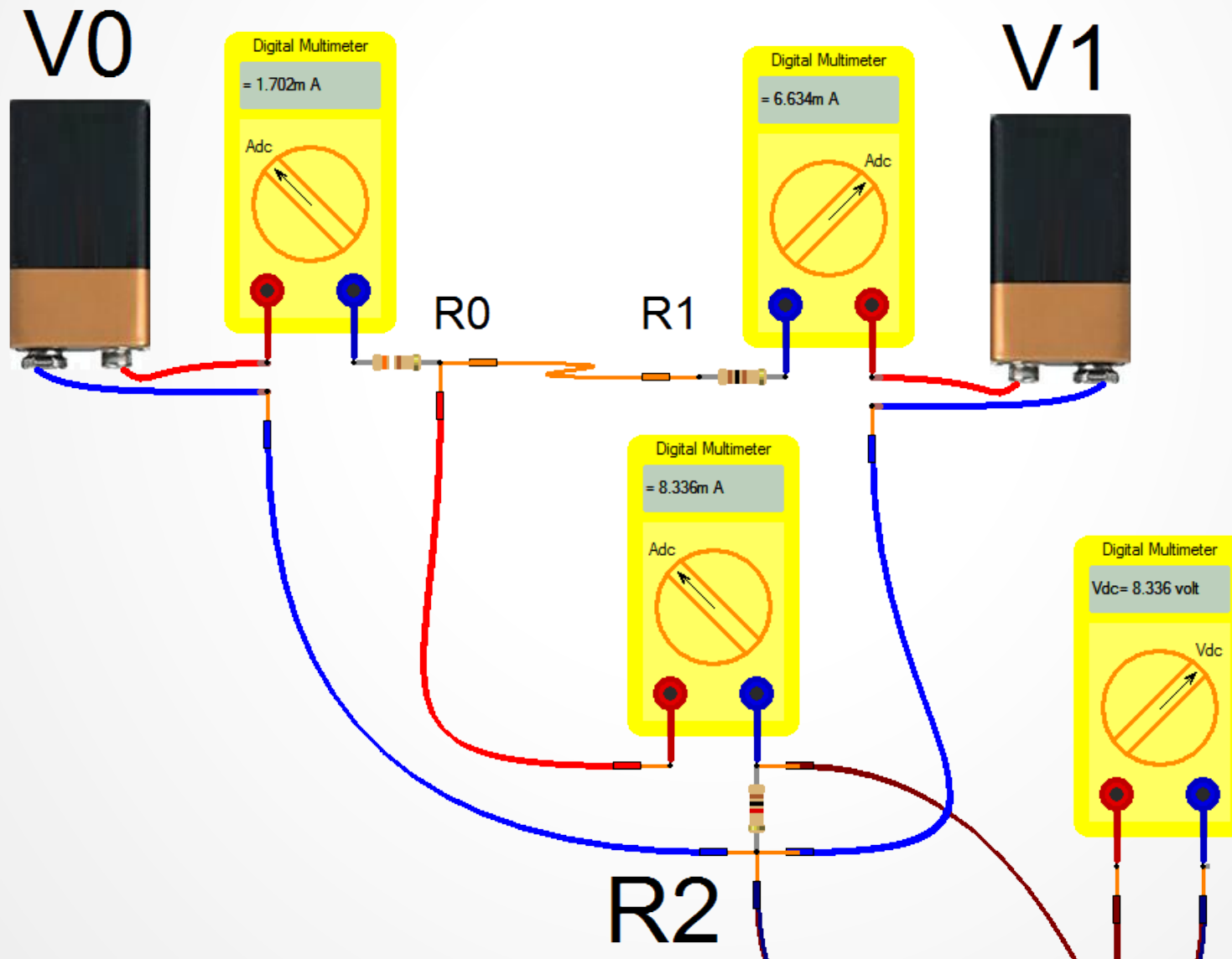- Depending on R0 and R1: battery power (V0 or V1)




Nominal voltage

- Regulate around nominal voltage

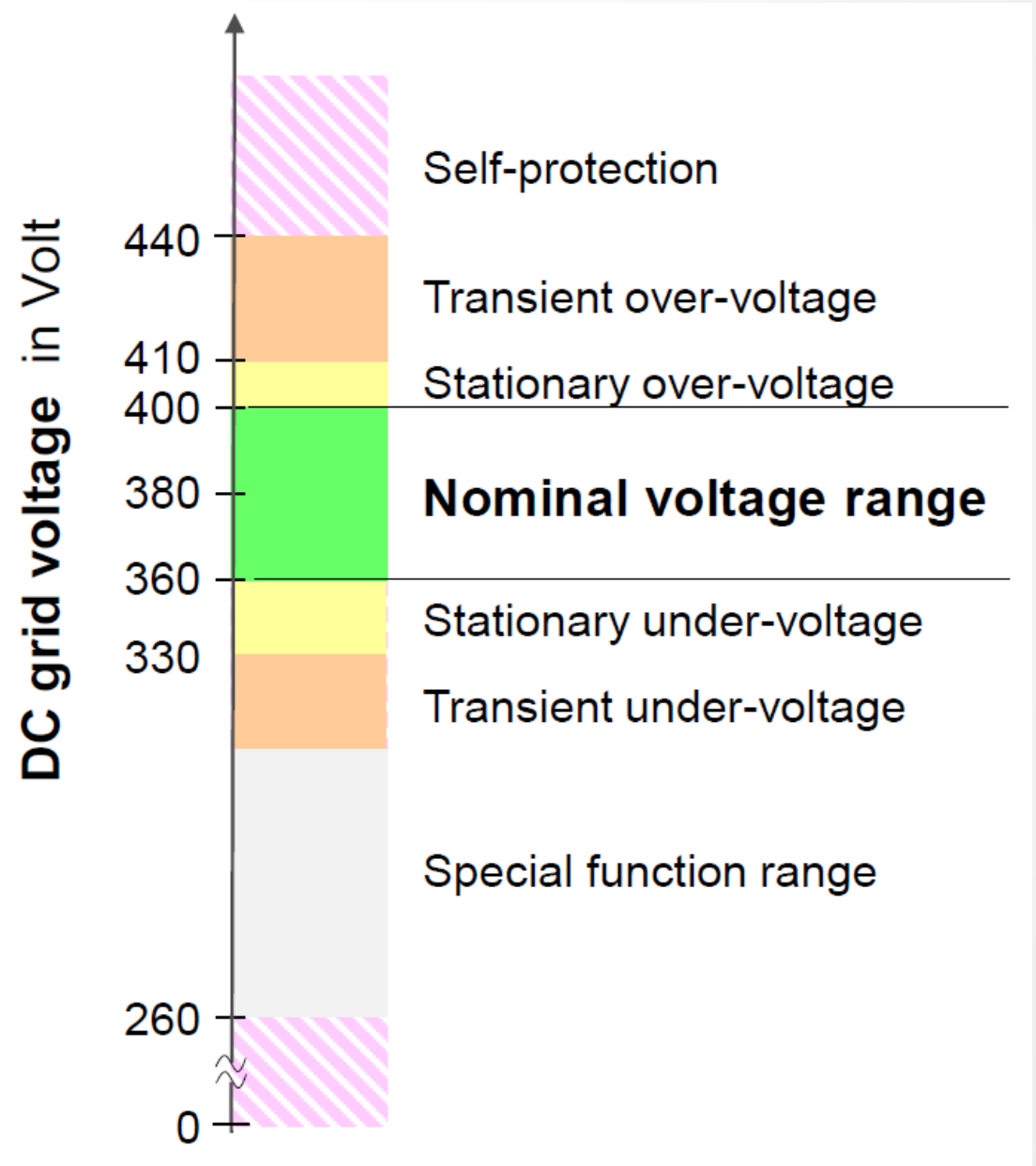


Droop control

- Control via the V_{grid} voltage

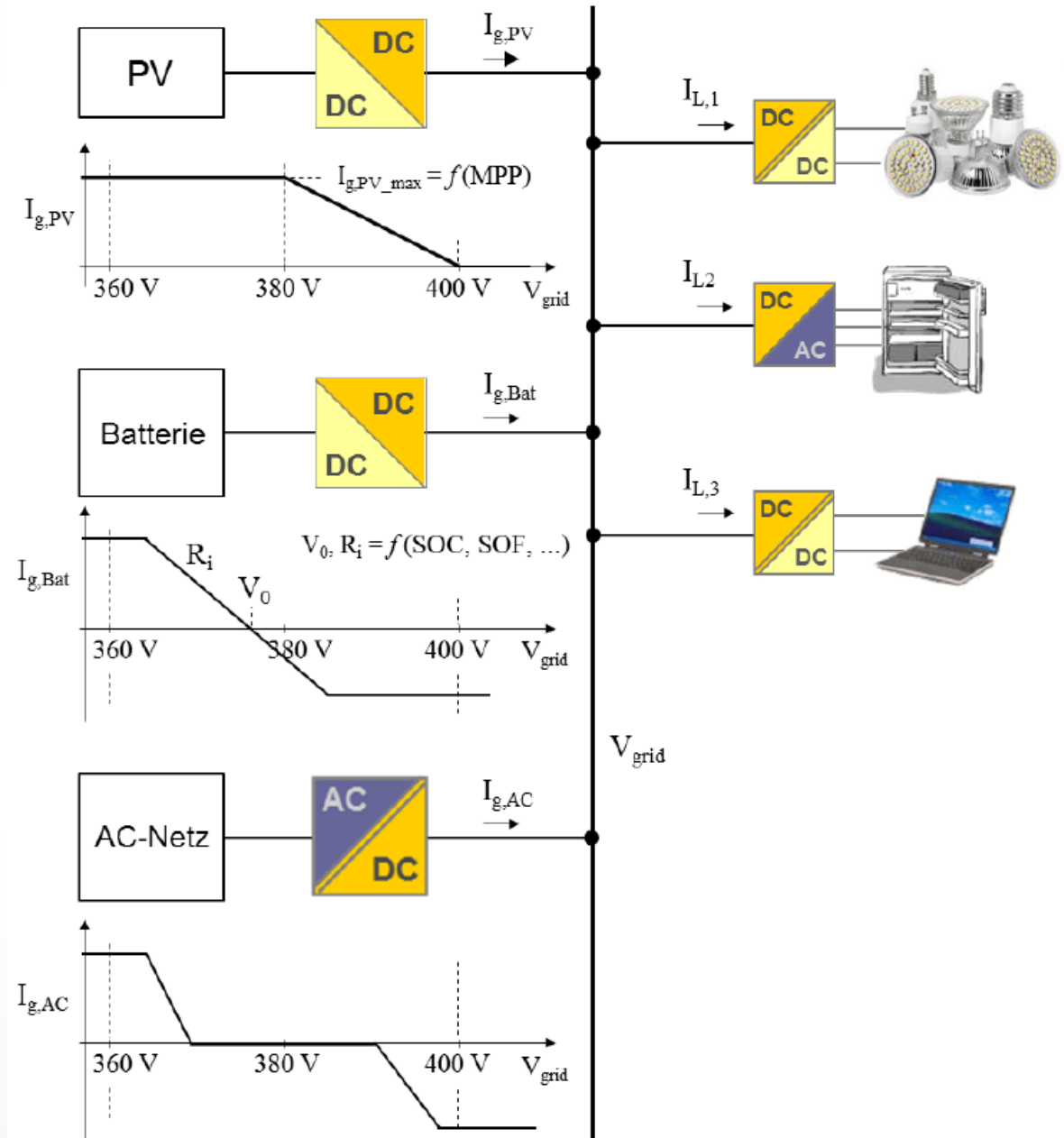


Without droop control

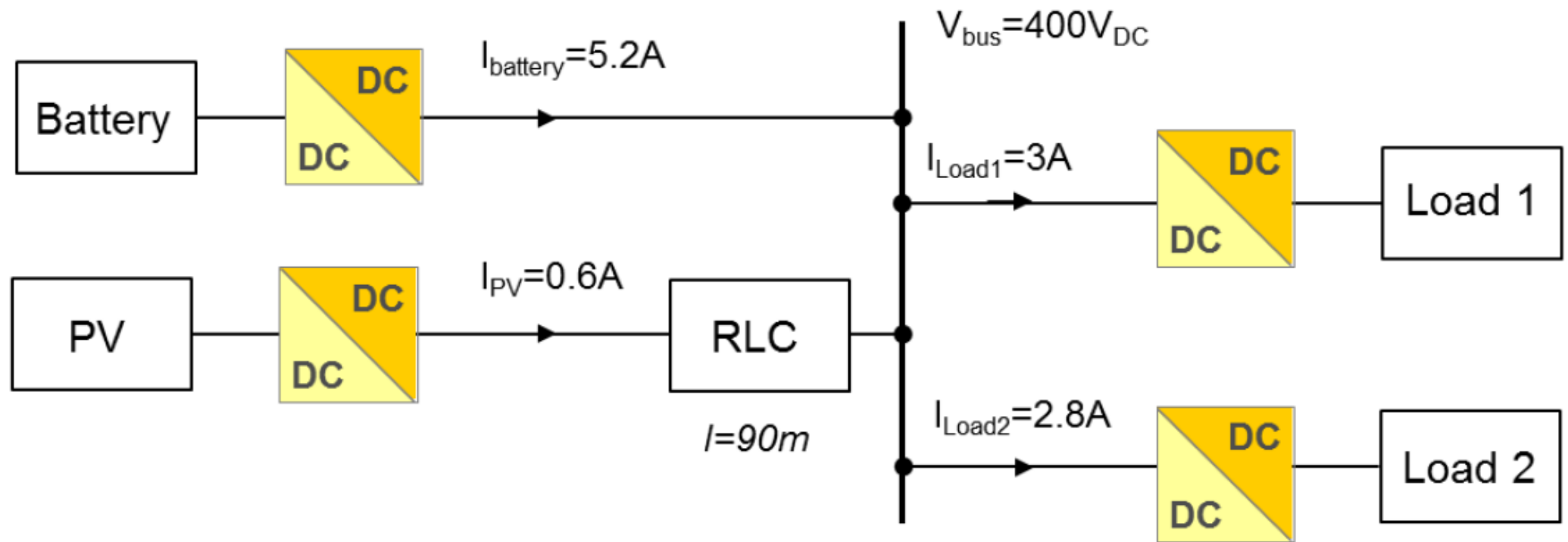- Most power is coming from the battery,
- Nearly nothing from the PV





With droop control

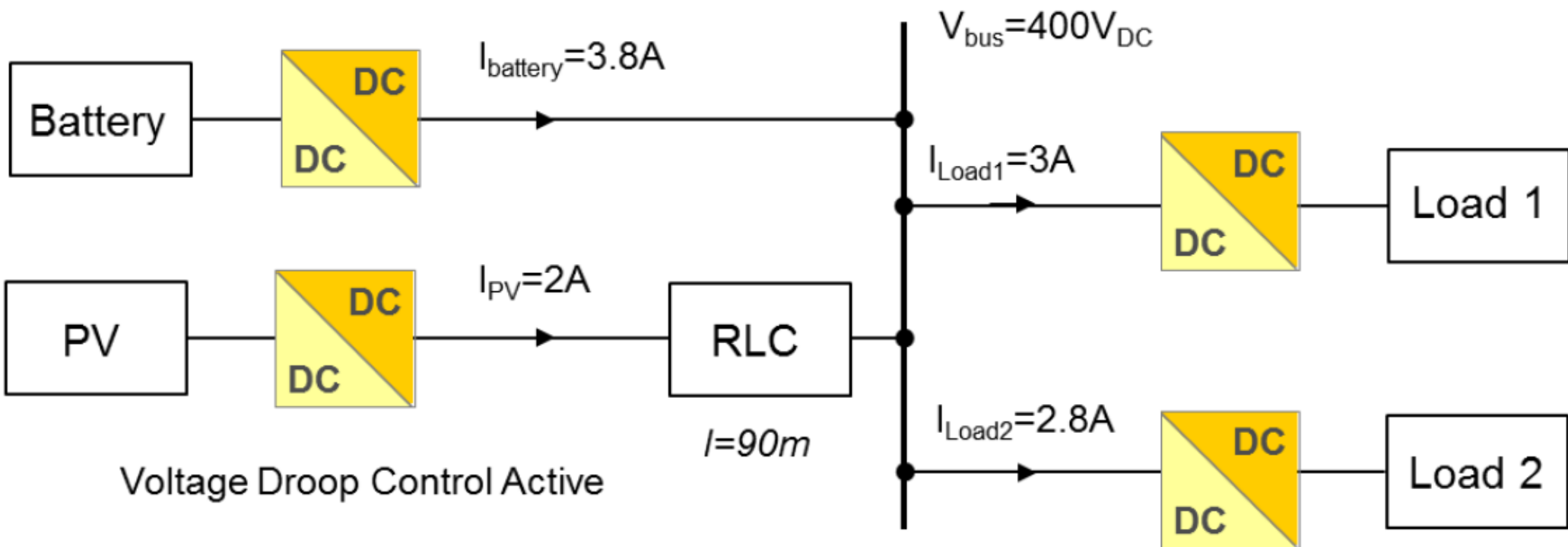- More equal power distribution
- The PV also delivers power




Drop characteristic

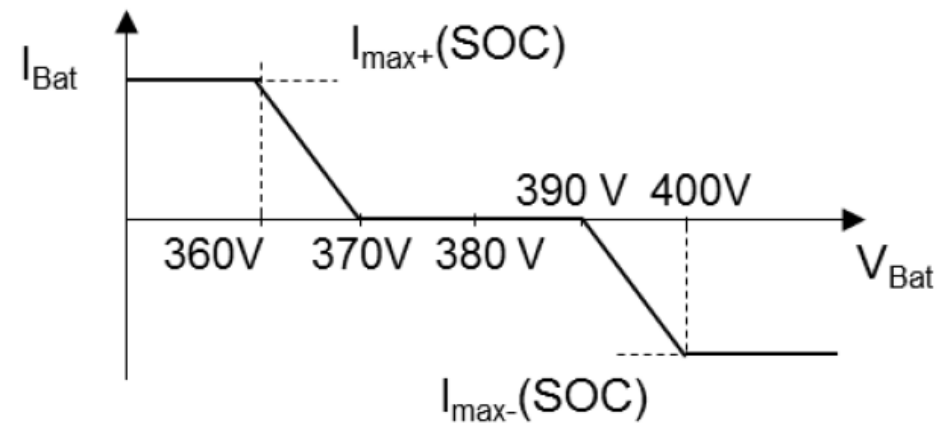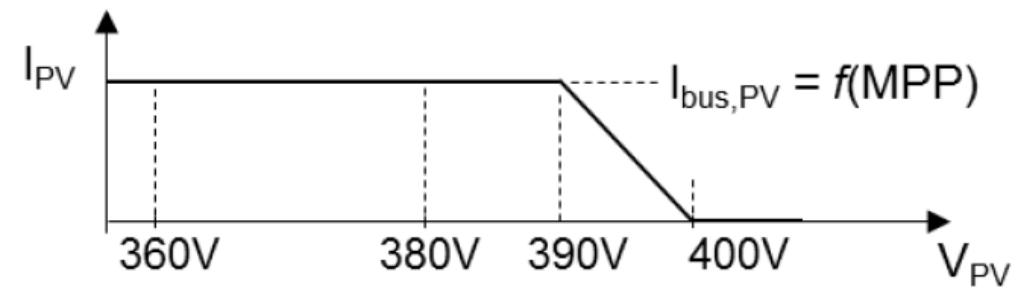
- Depending on V_{bus} :
 - we select the load current




Grid Connection

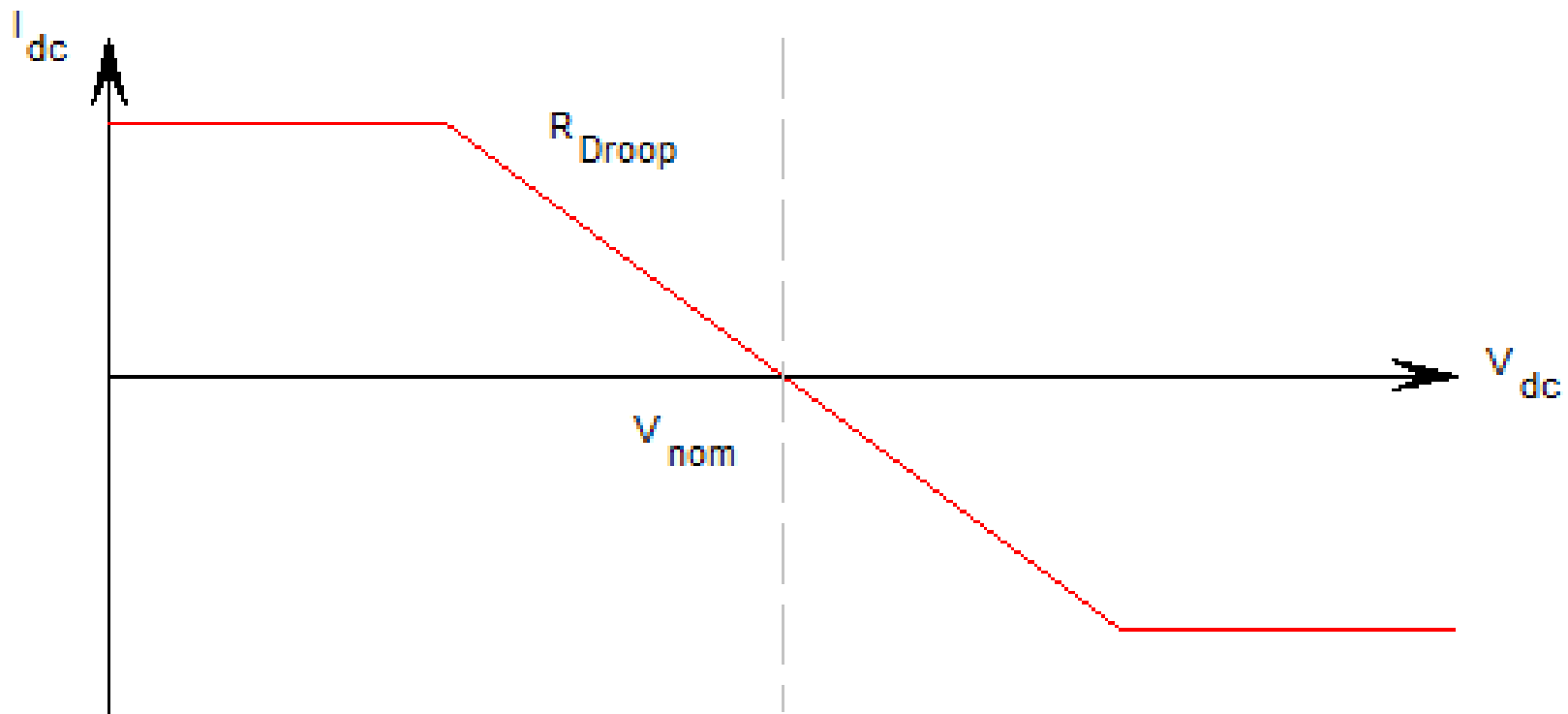


Battery

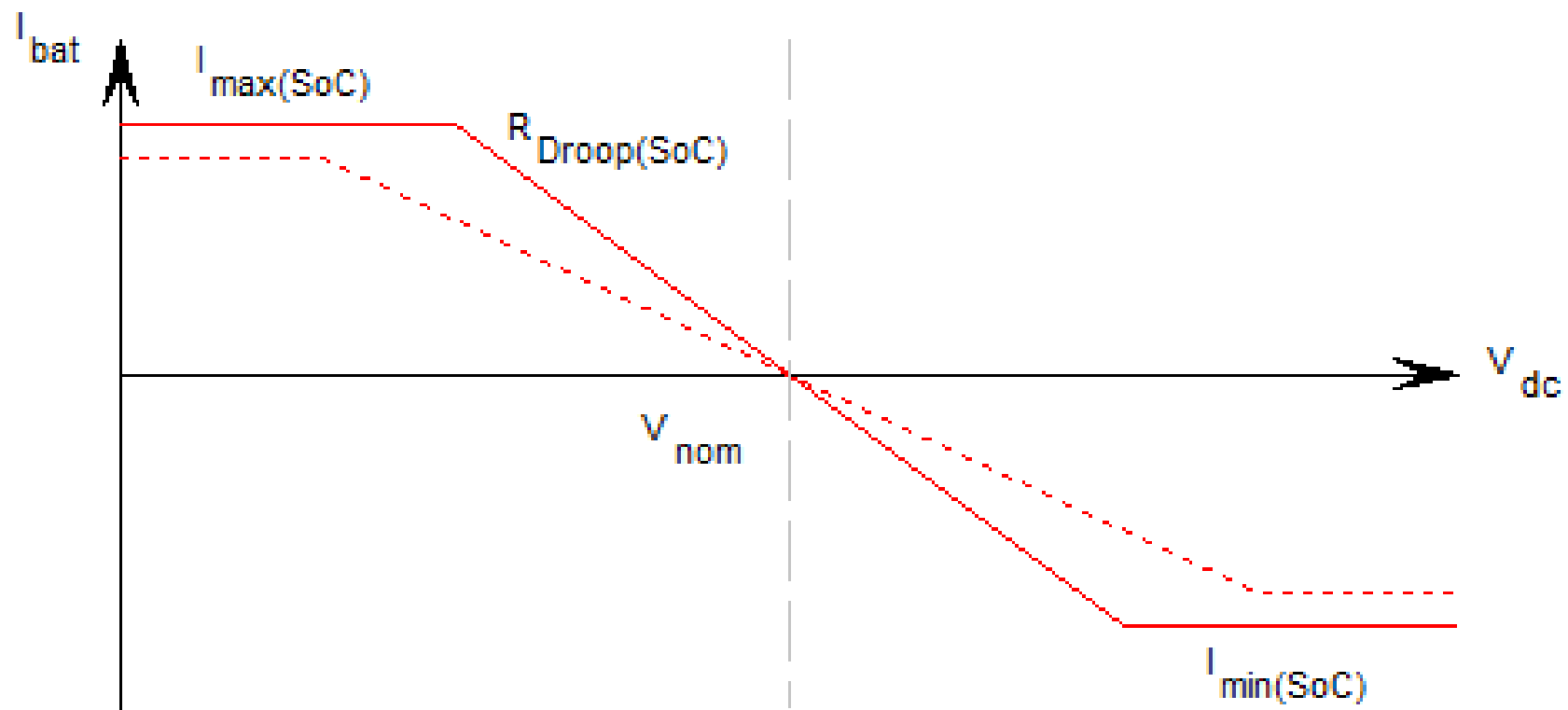


Solar

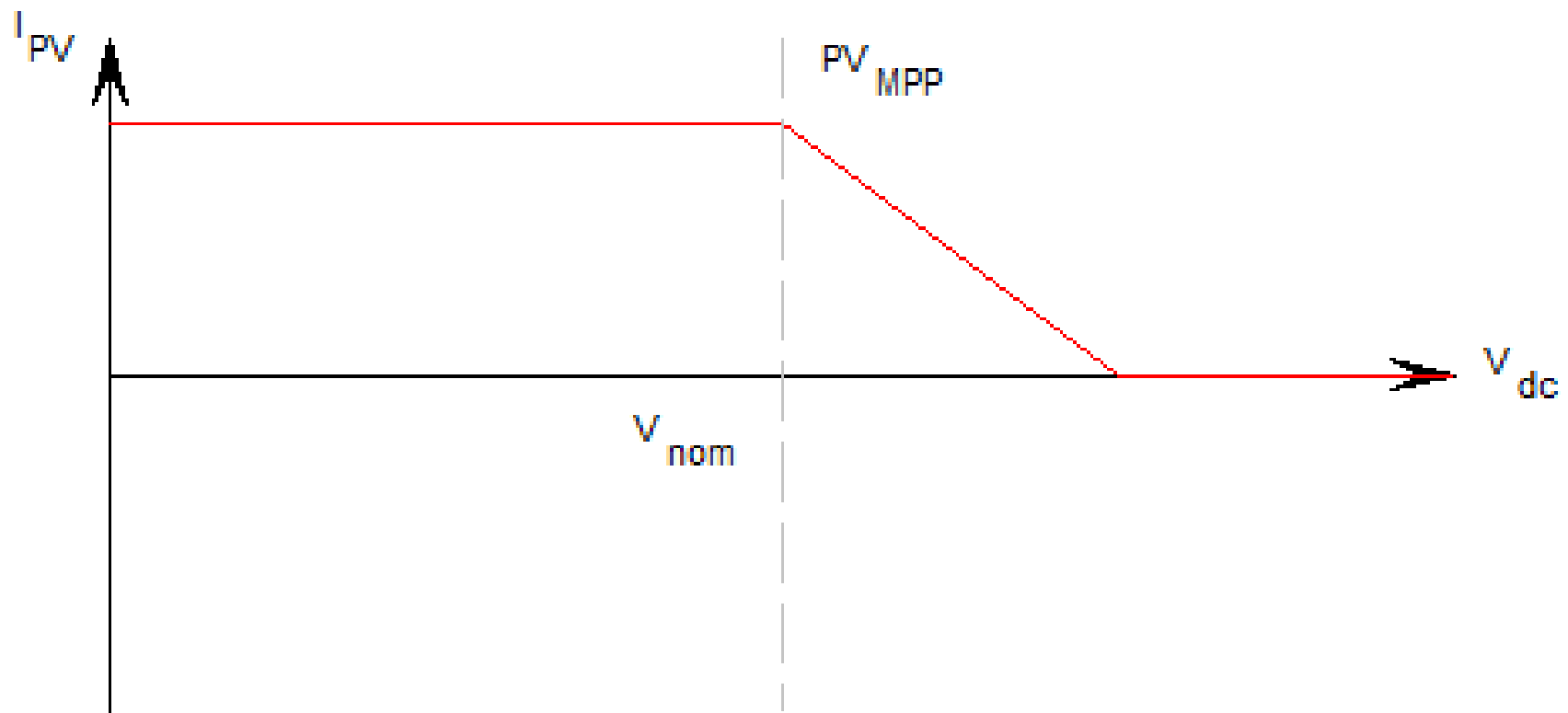

Solar and other sources

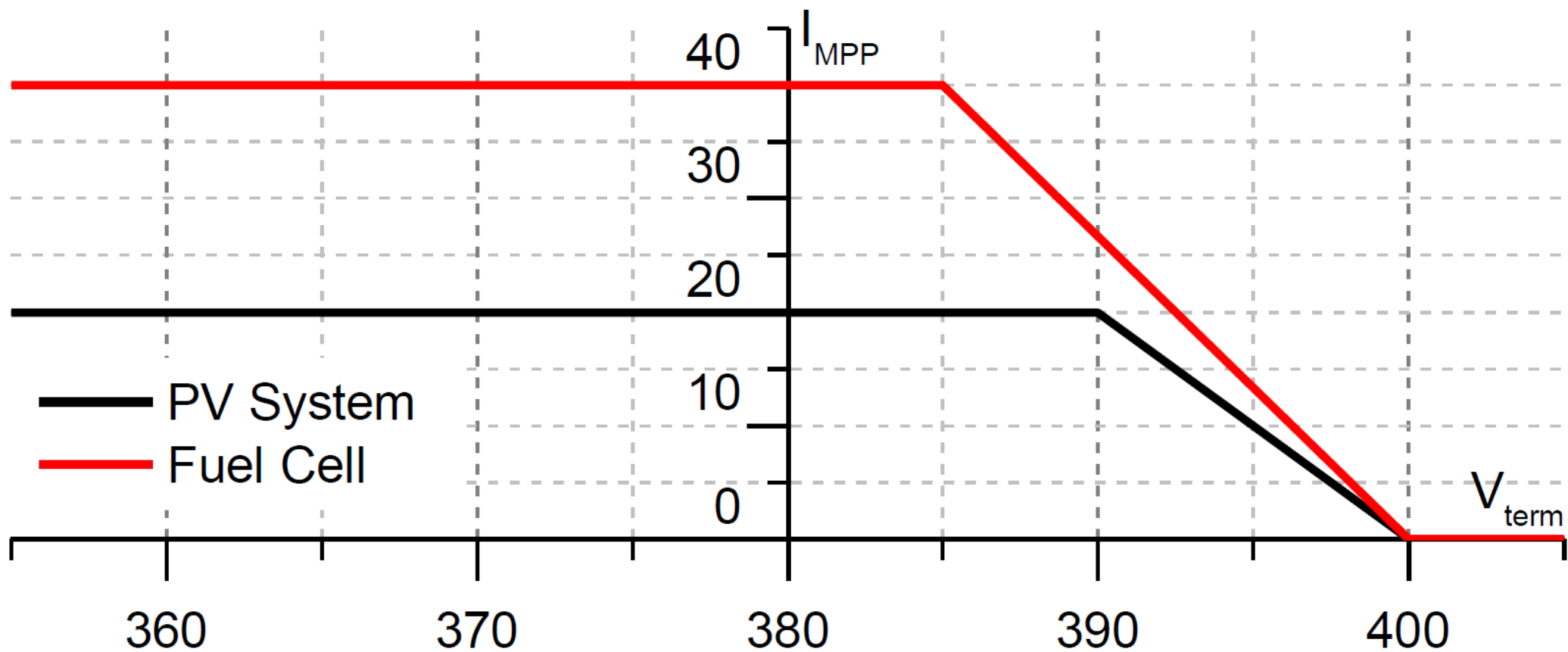


Grid and battery storage

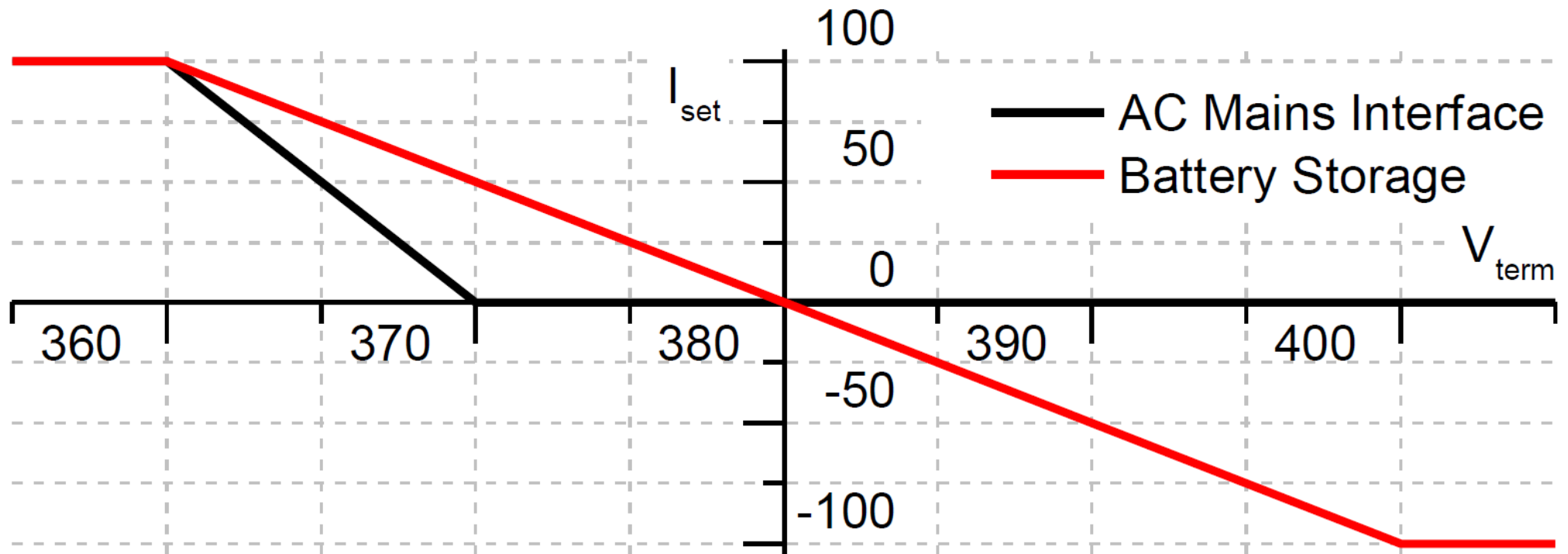

Power Electronics

Casroc

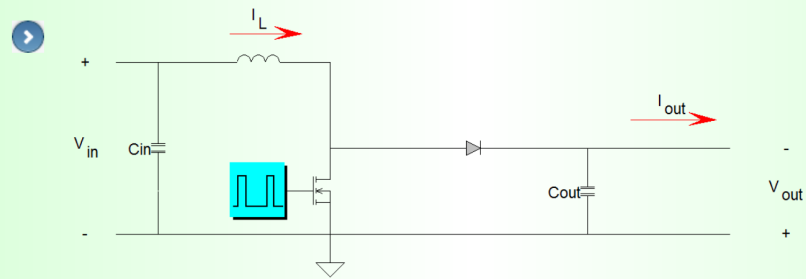


Input voltage	20	[V]
Output voltage	30	[V]
Output current	0.551	[A]
Inductor current ripple	40	0..100[%]
Output voltage ripple	0.1	0..100[%]
Switching Frequency	57.5	[kHz]
Diode forward voltage drop	0.7	[V]
Use predefined inductor value, (leave 0 for suggestion)	150	[μH]

Calculate


Grafiek Outputfields tab3 tab4 tab5

$L=150[\mu\text{H}]$ $C=58.56[\mu\text{F}]$ $T_{\text{on}}=6.06[\mu\text{s}]$ $T_{\text{off}}=17.39[\mu\text{s}]$ $I_{\text{peak}}=1.25[\text{A}]$
 $i_{\text{ripple}}=0.81[\text{A}]$ $V_{\text{ripple}}=0.03[\text{V}]$ $i_{\text{in}}=0.85[\text{A}]$


Gate signal for the Mosfet:

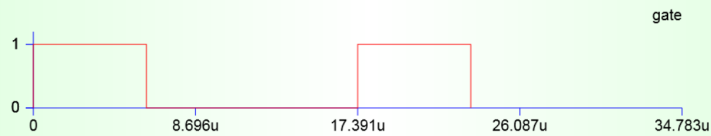


Current through the inductor:

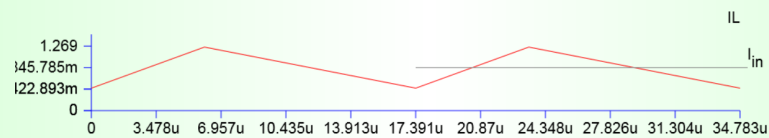


No common ground!

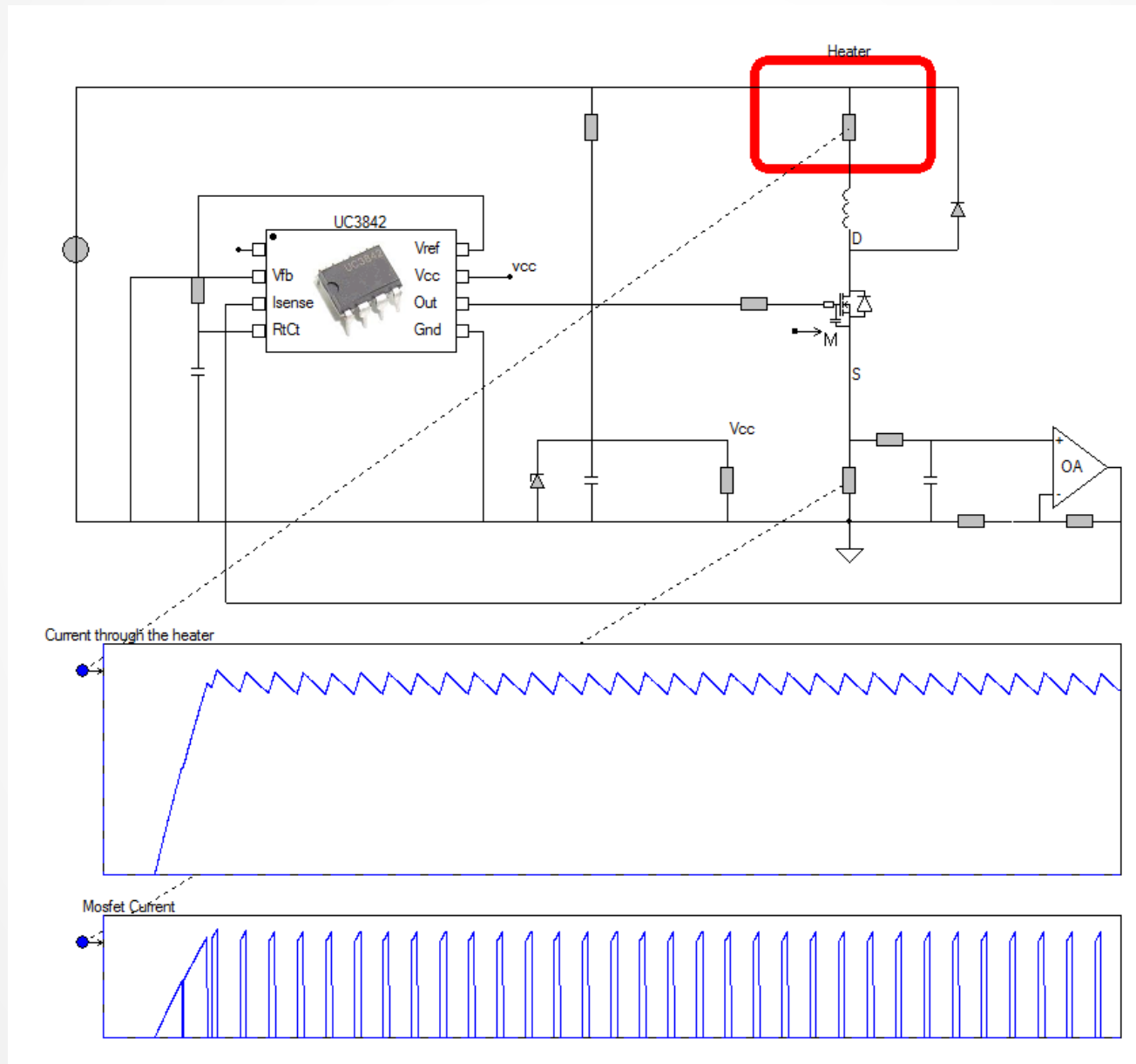

Grid manager

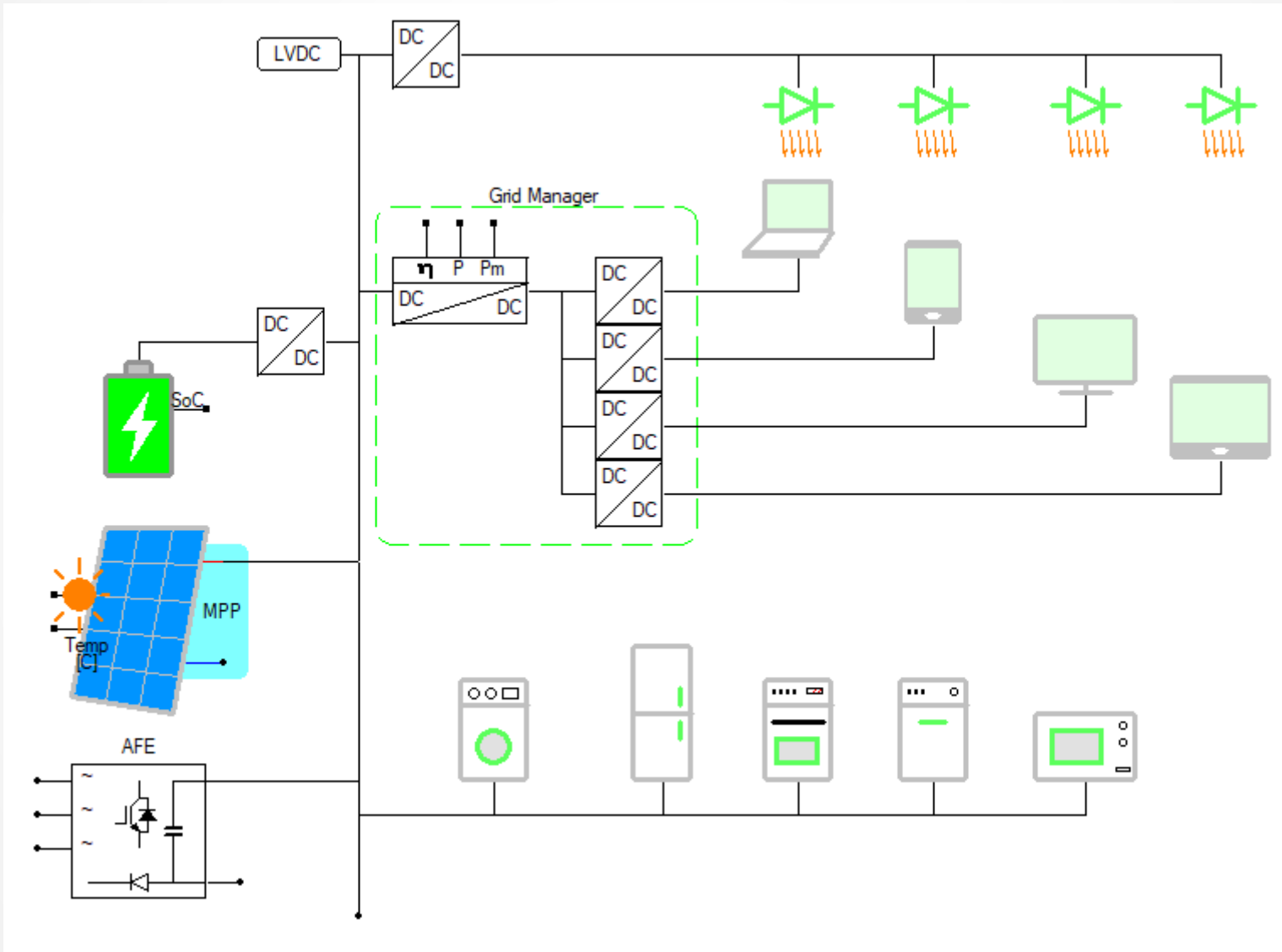


Synchronous Buck converter

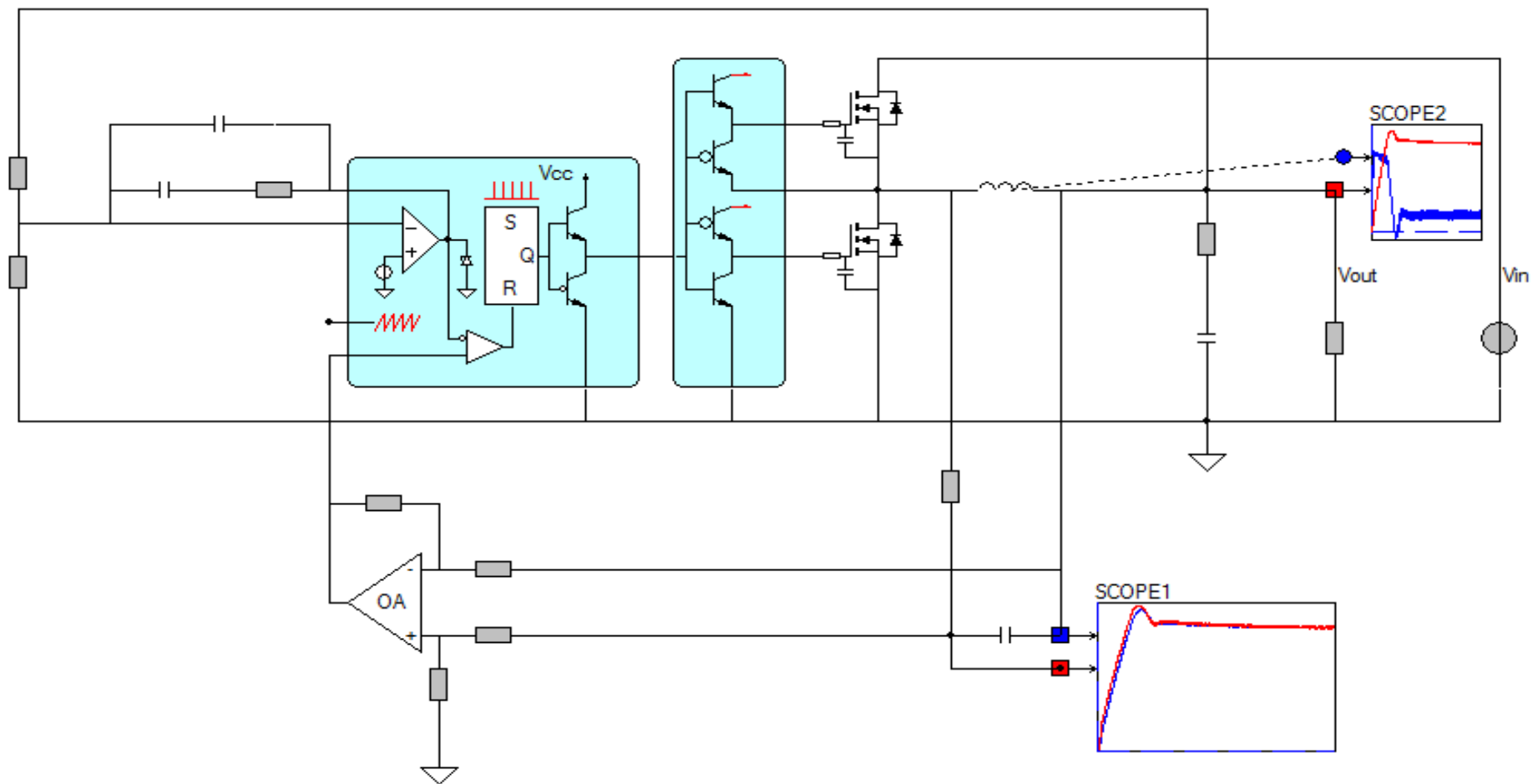


Current measurement

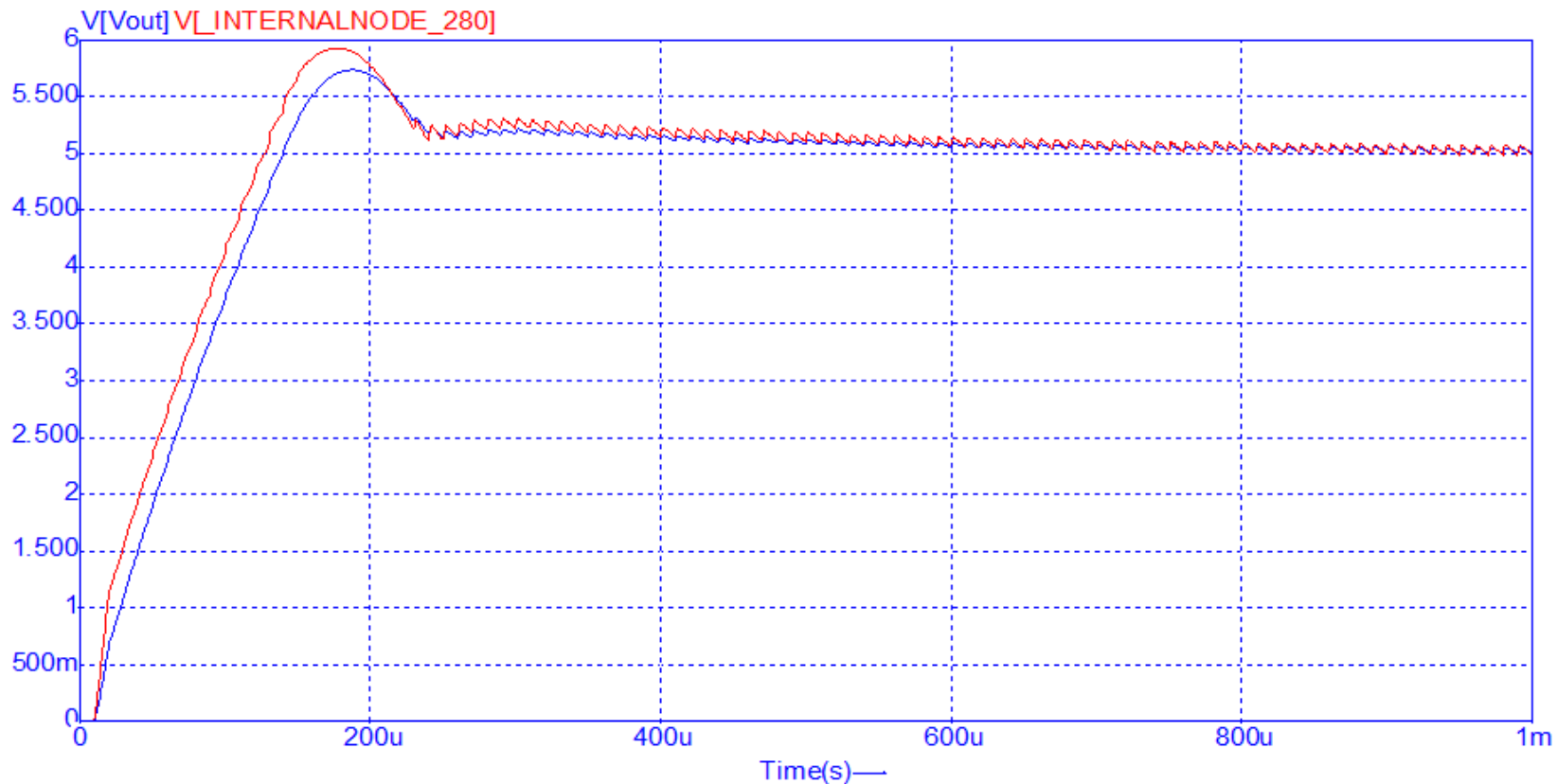- Current is measured as:
 - Differential voltage over a shunt resistor!
 - Shunt resistor: Series resistance of inductor!









Current is controlled!

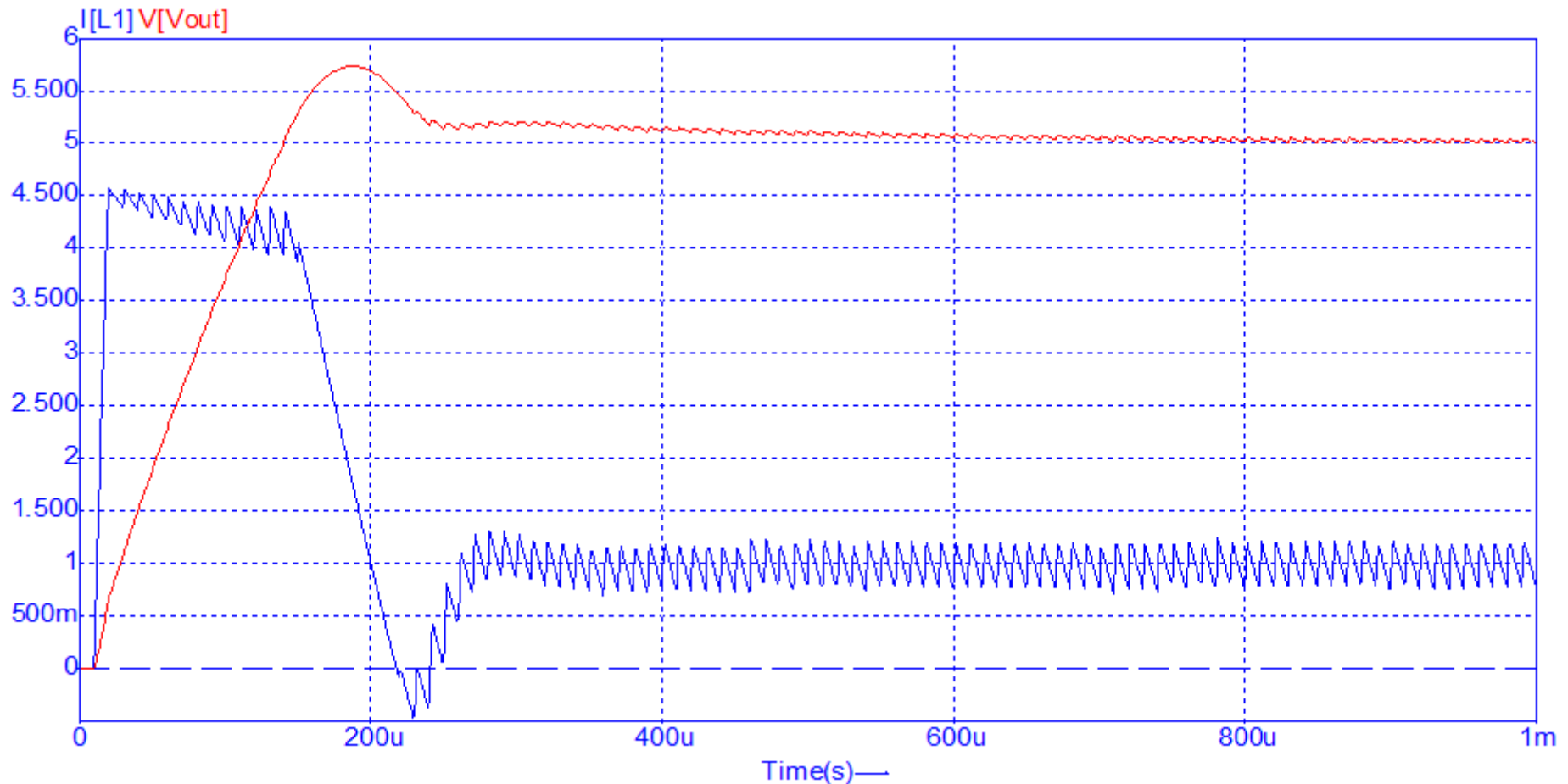
- Only current through inductor can be controlled!





Bidirectional DCDC converter

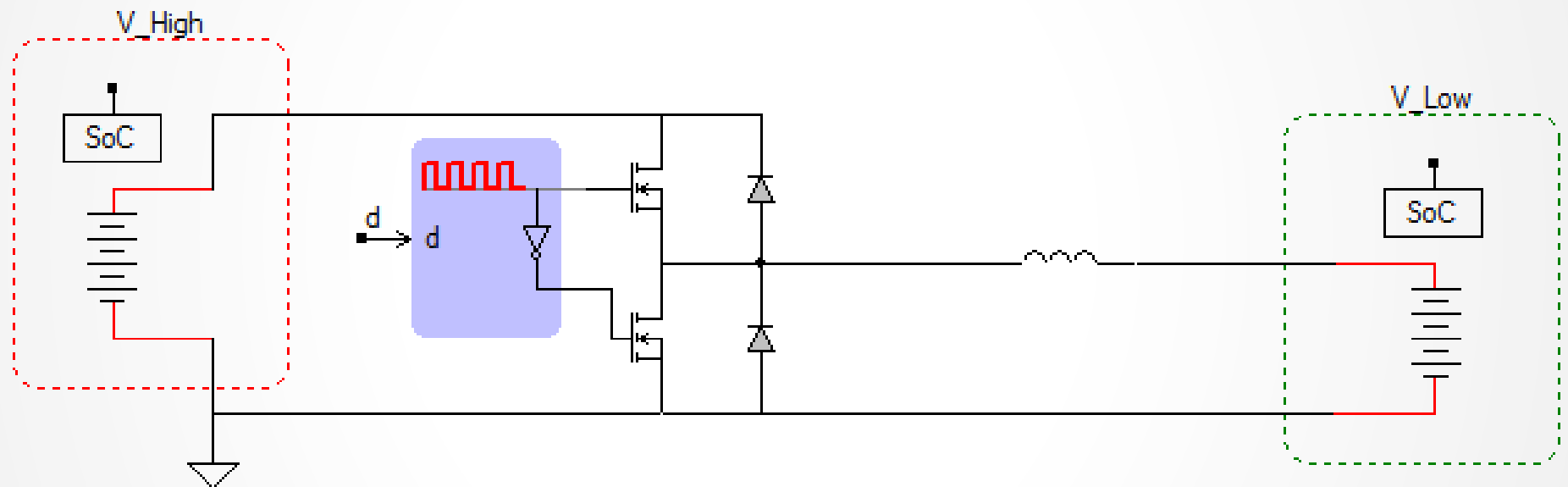


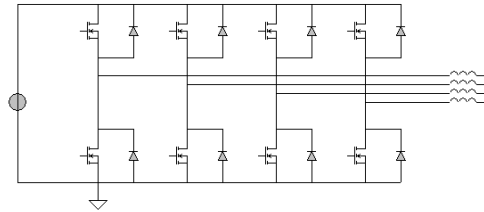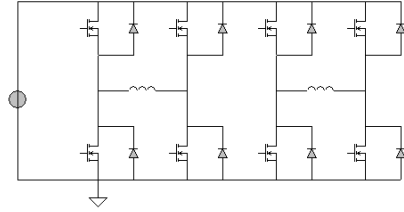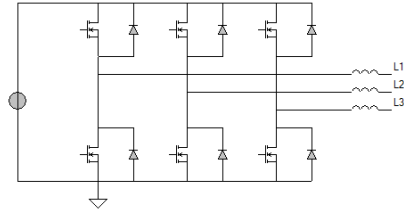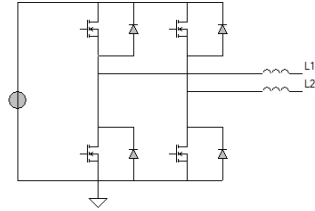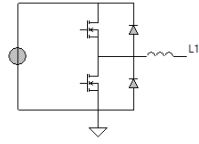


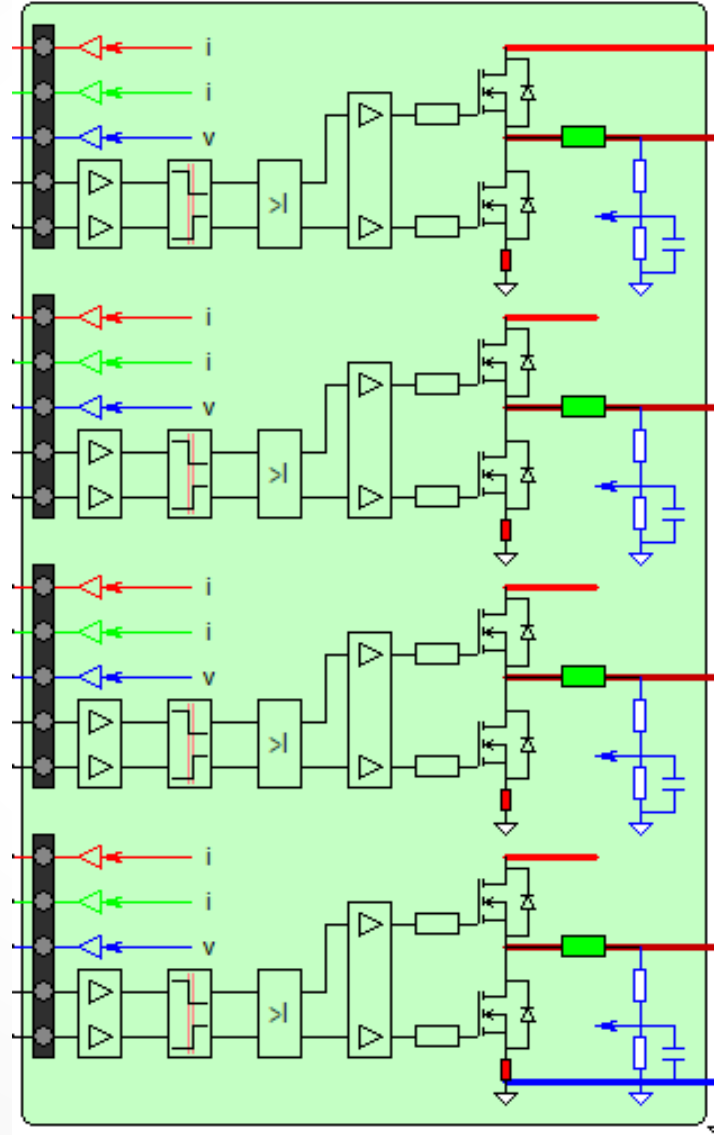

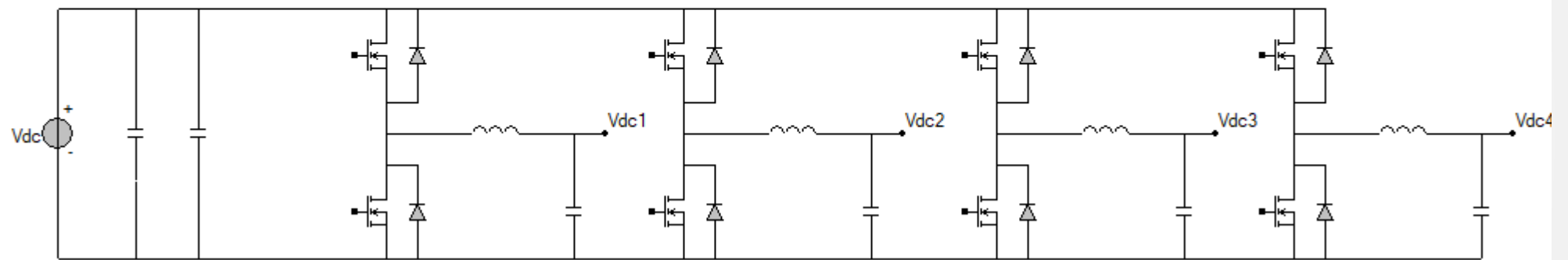

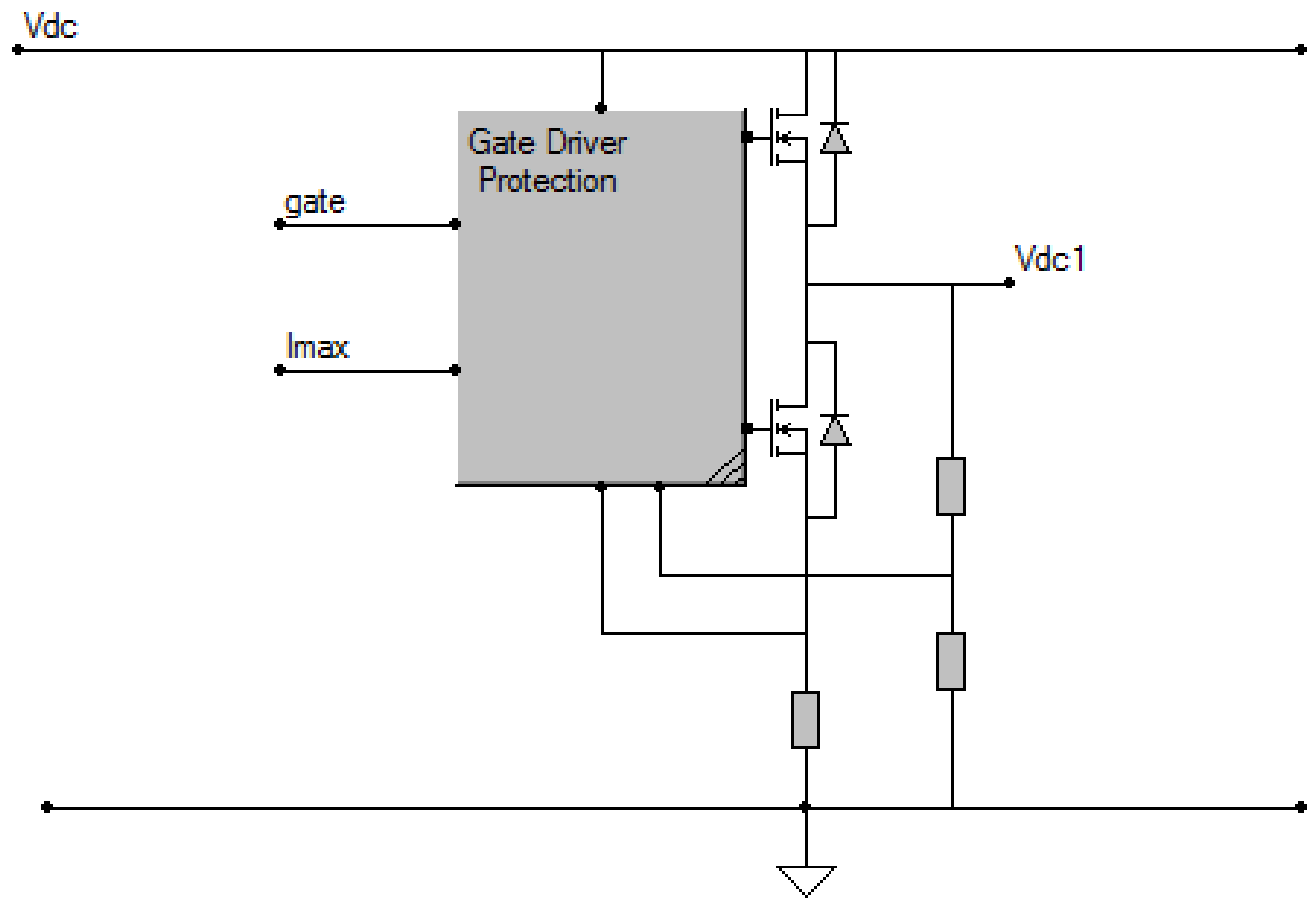

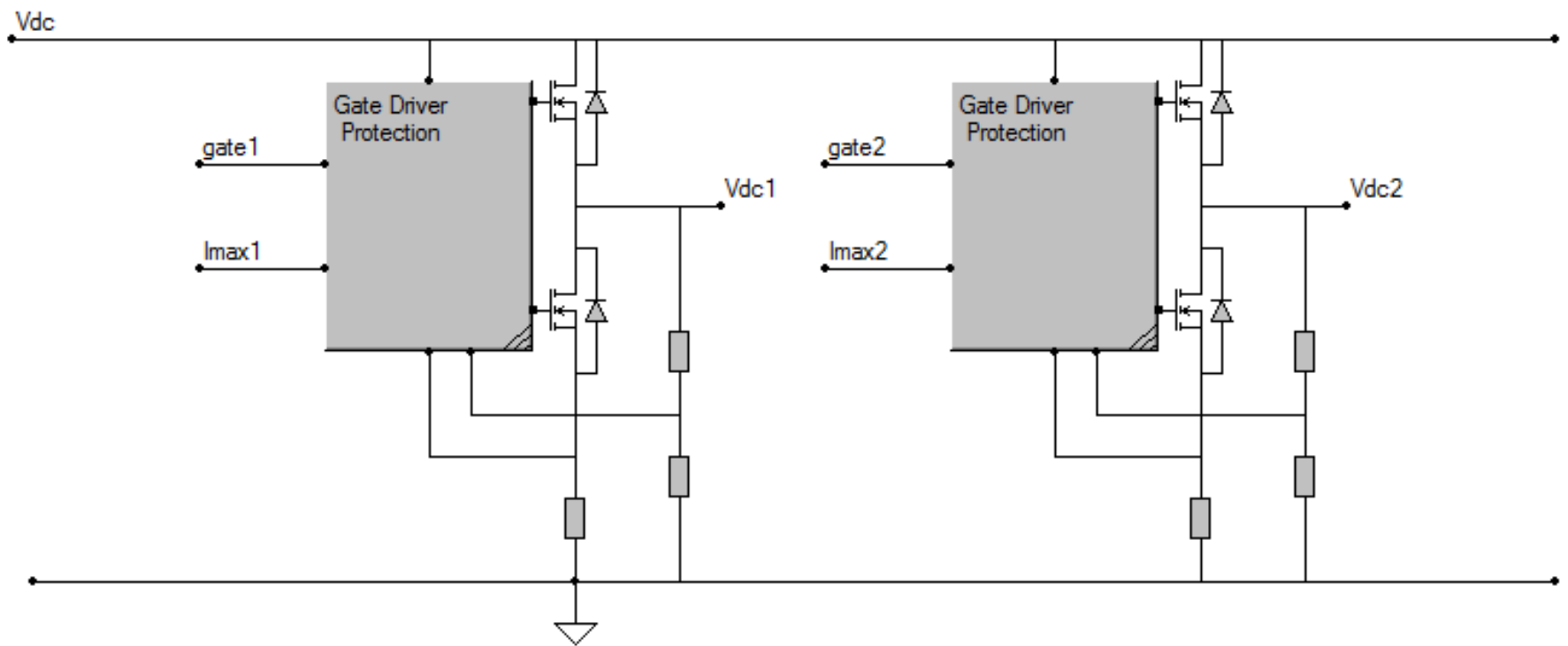

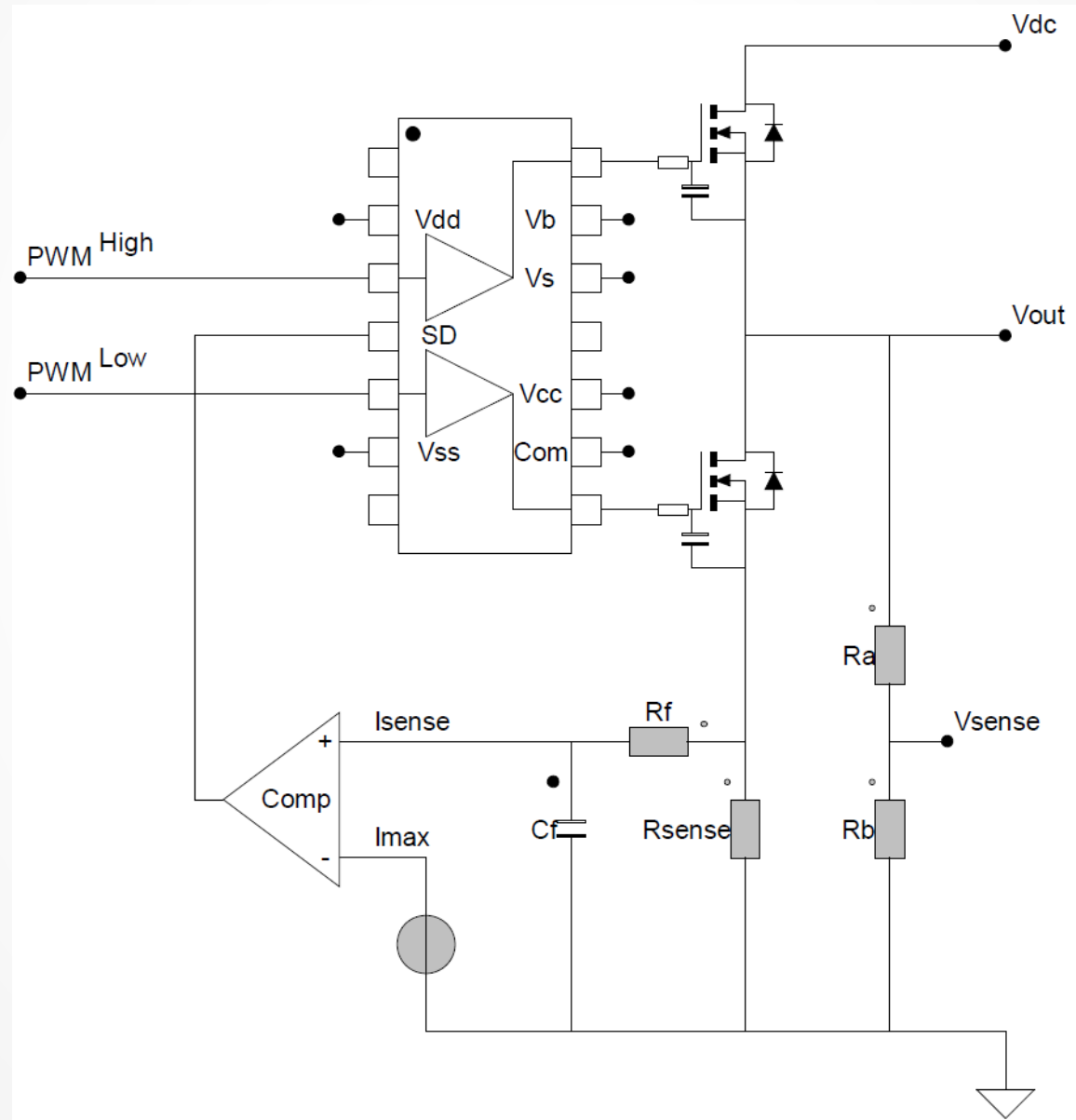


Fraunhofer Grid Manager





Bidirectional converter Dual Active Bridge

350-400 volt


48 volt

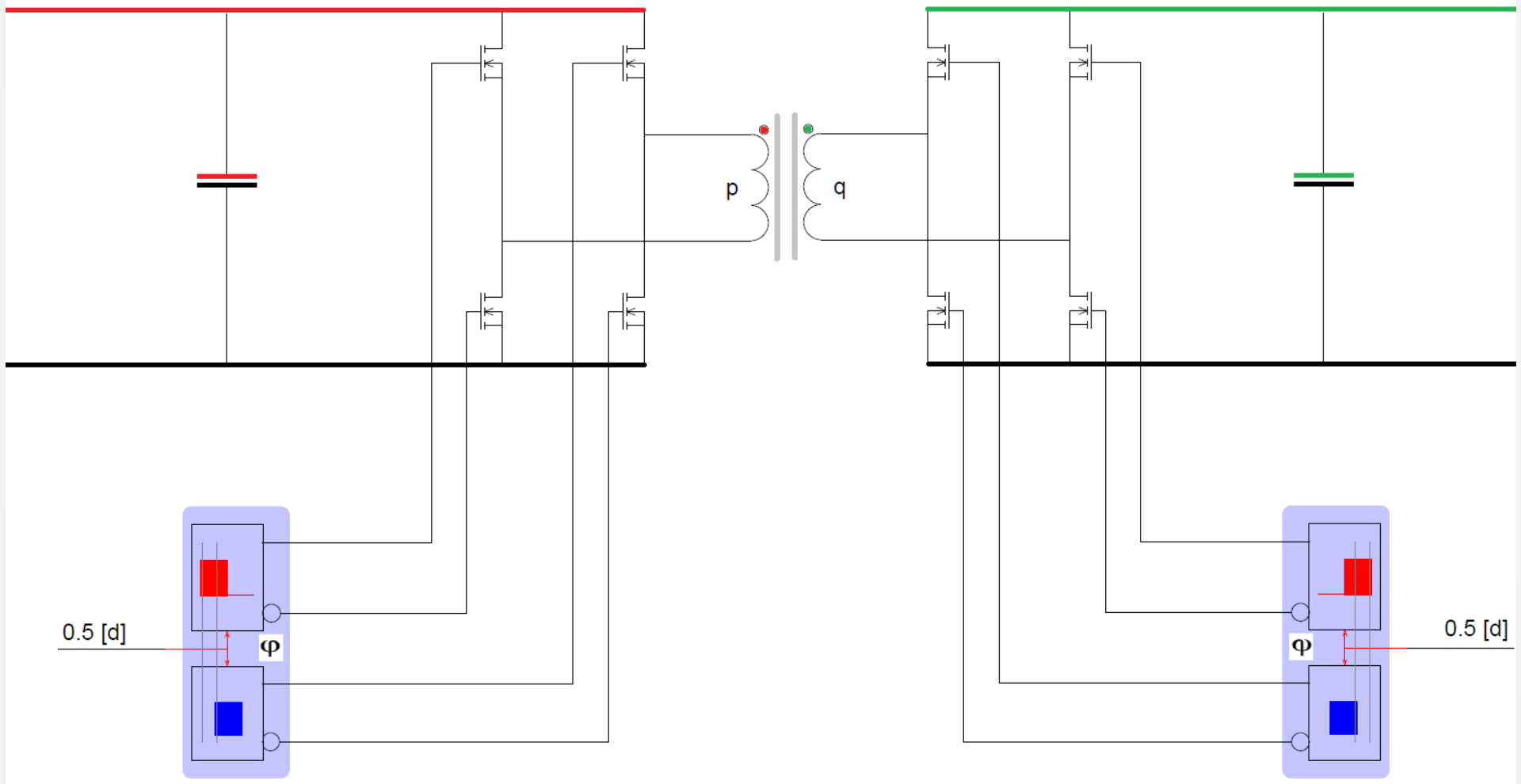


Bidirectional Flyback

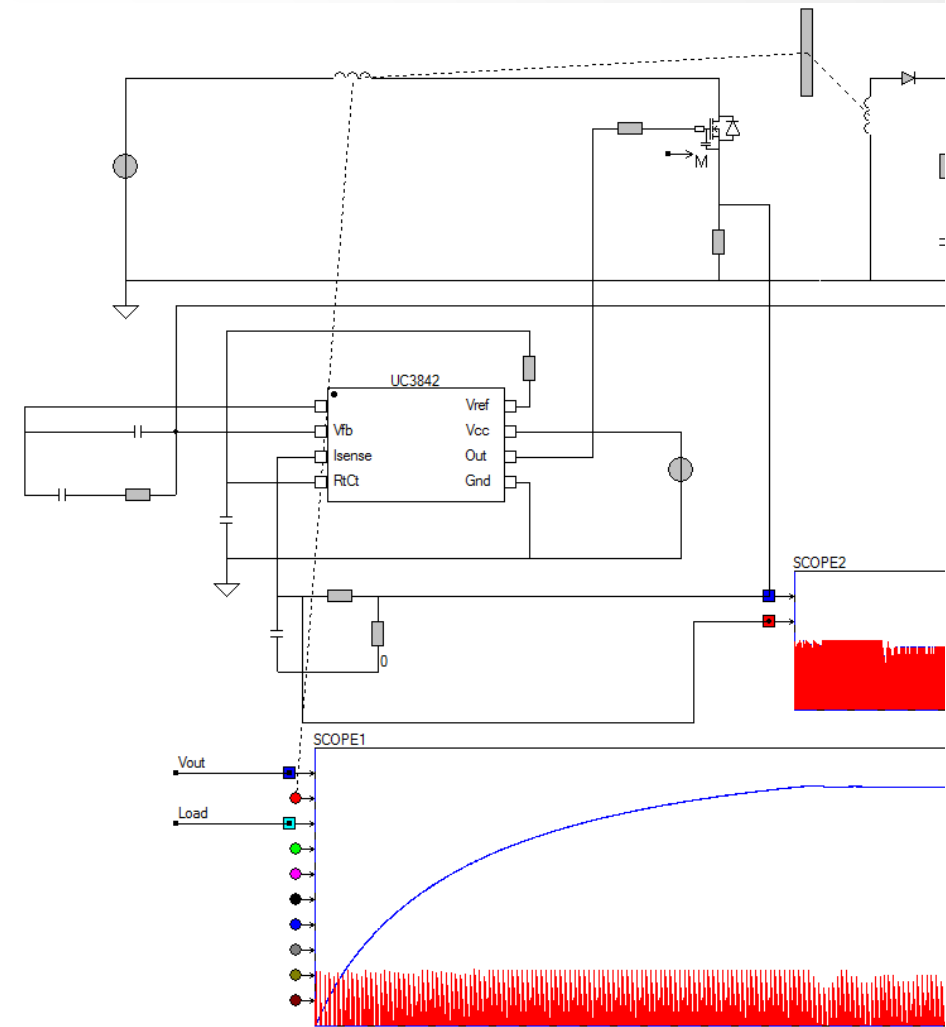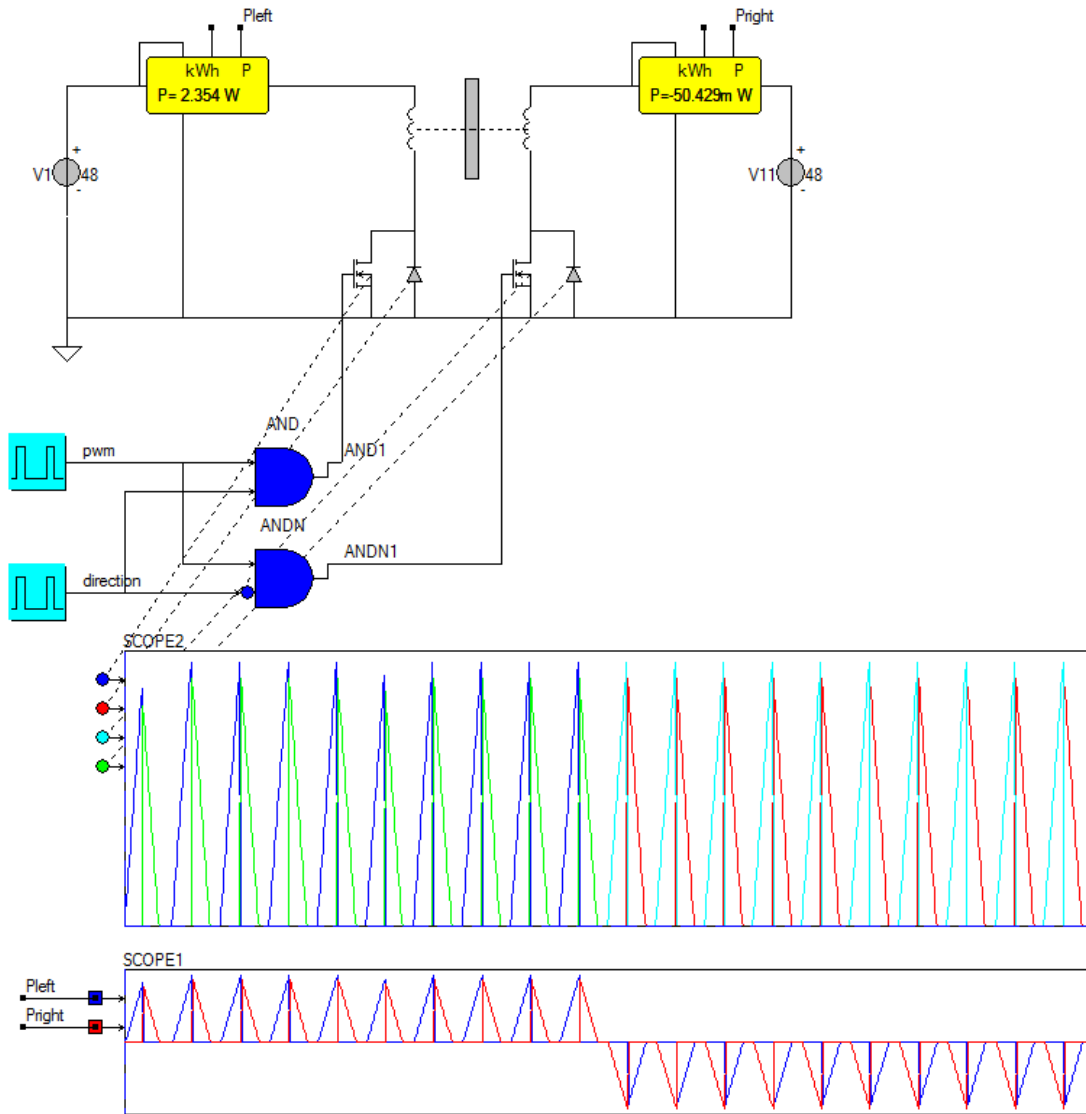

Flyback battery droop control

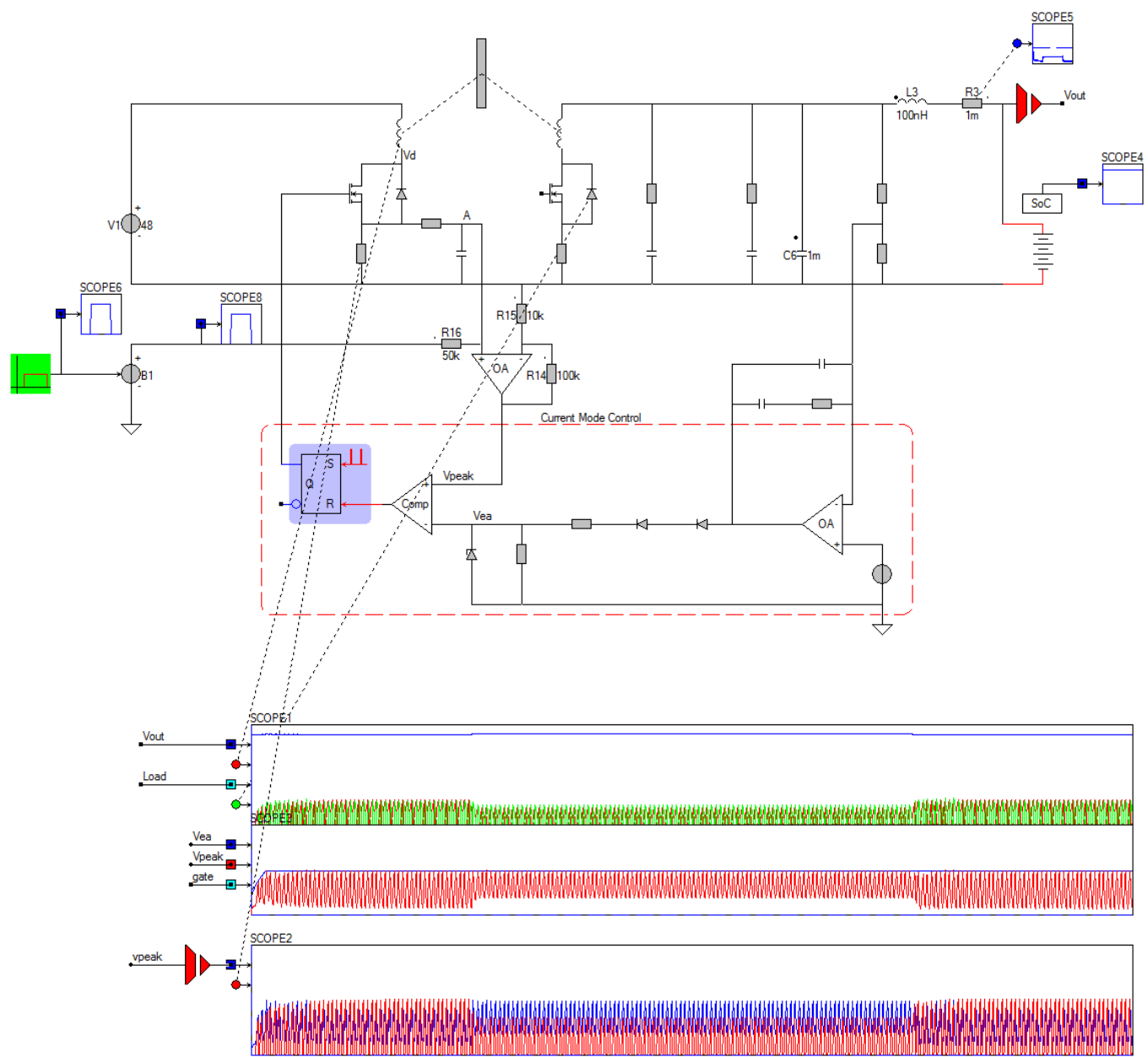


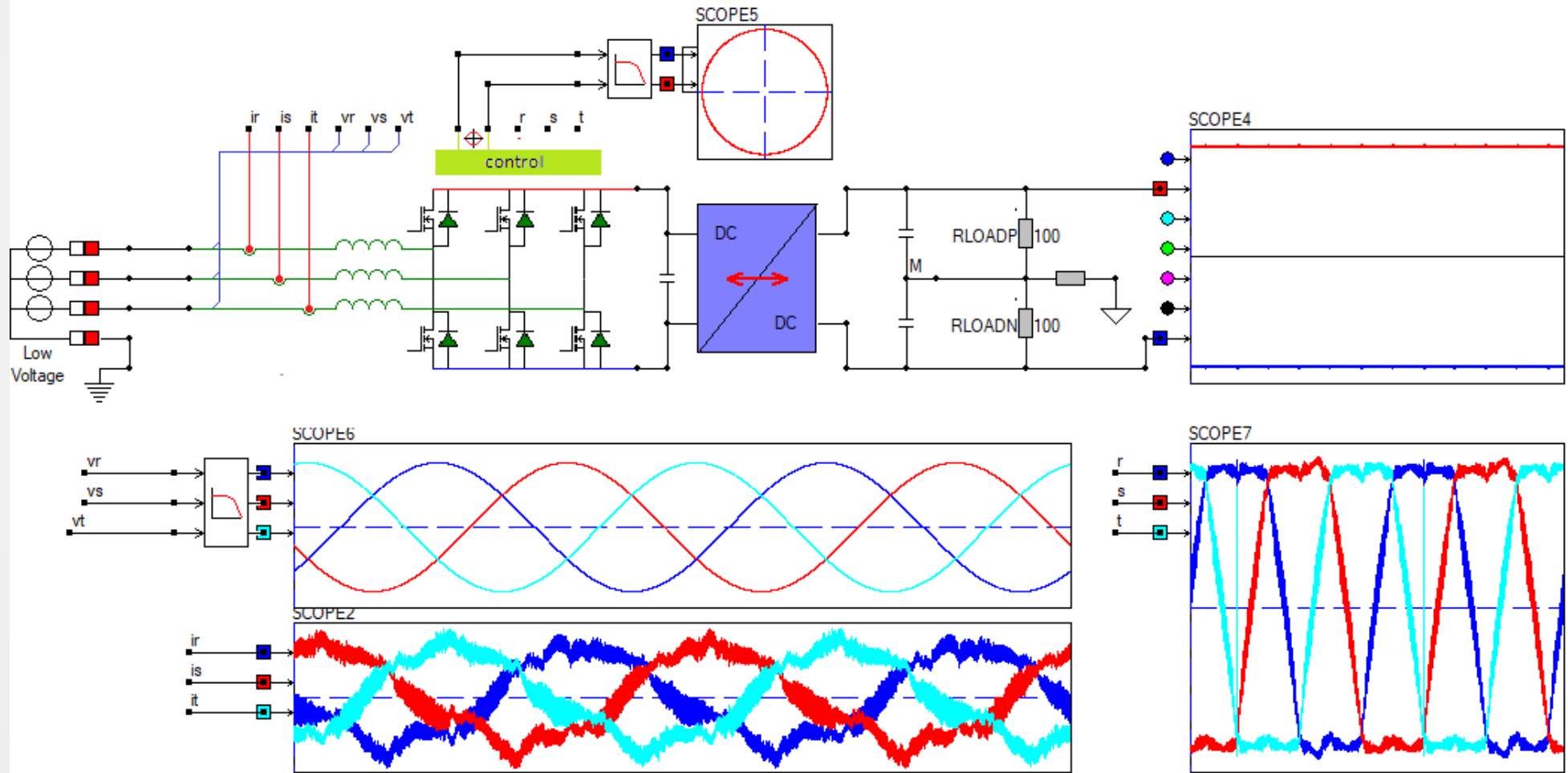Interfacing AC and DC Bidirectional : Active Front End




Connecting two DC grids

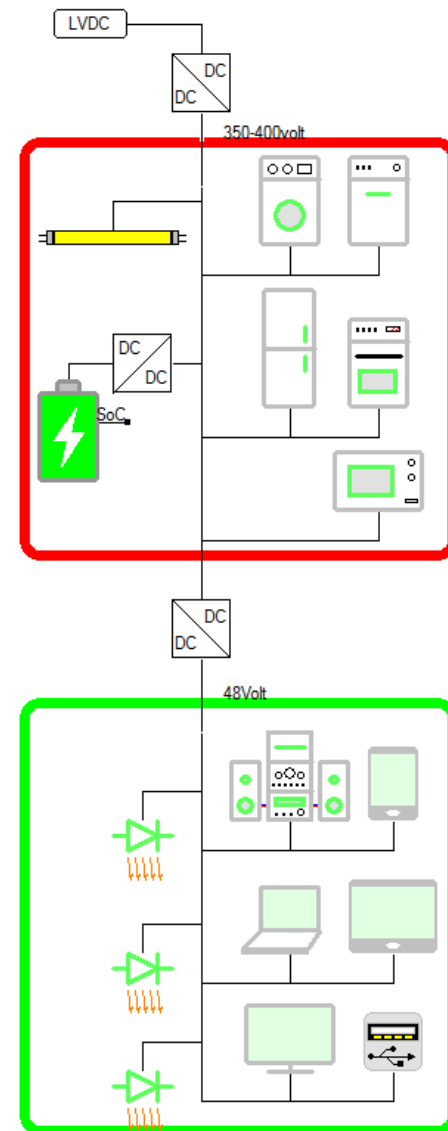
- High power 350-400volt grid
- Low power 48 volt grid



AFE & Dual Active Bridge

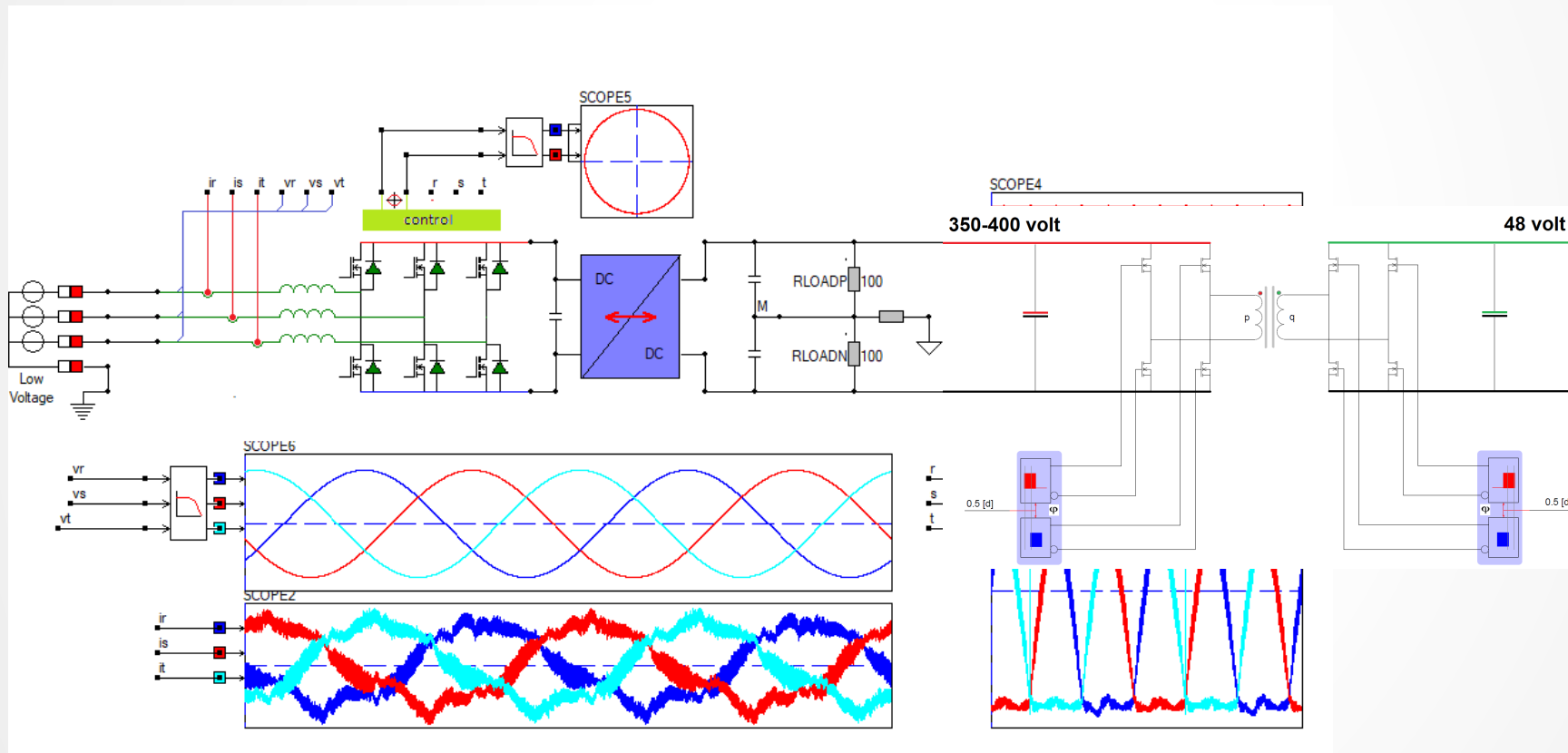

Drift control

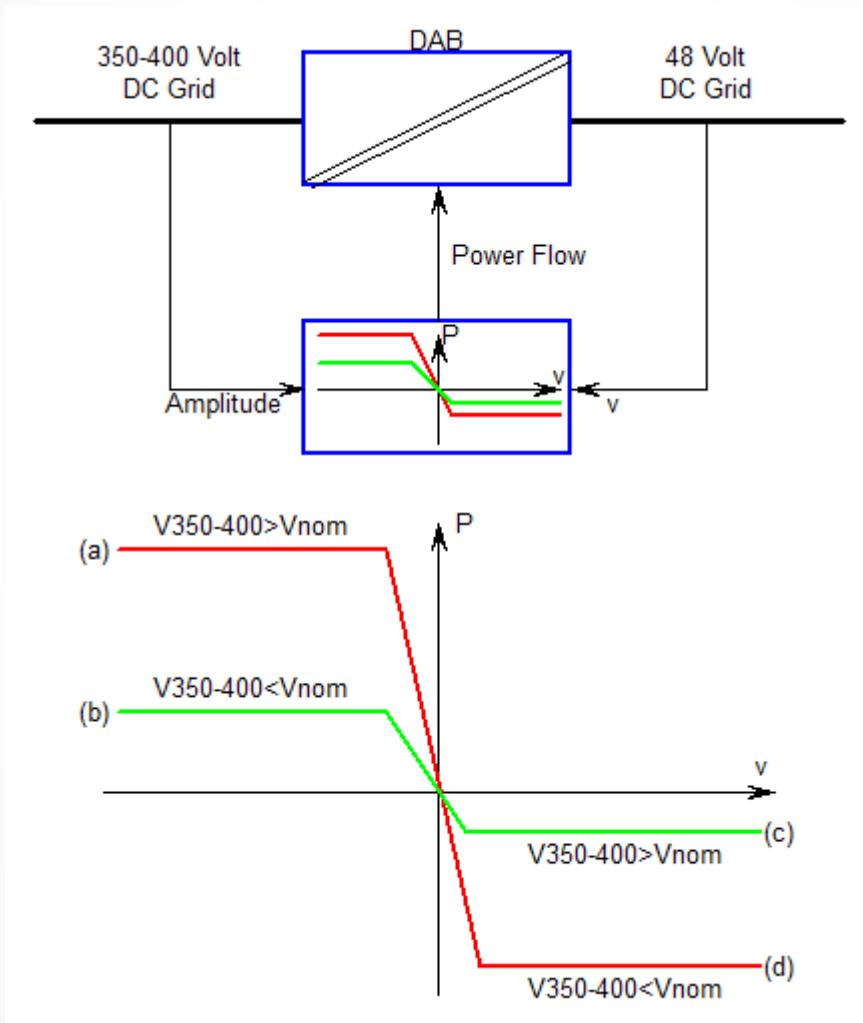

Conclusion

- Control
 - With communication?
 - Without communication
- Droop control
 - D bus voltage
 - Power Electronics
 - Congestion Management

Questions?

www.caspoc.com/news/workshops/dctrees

