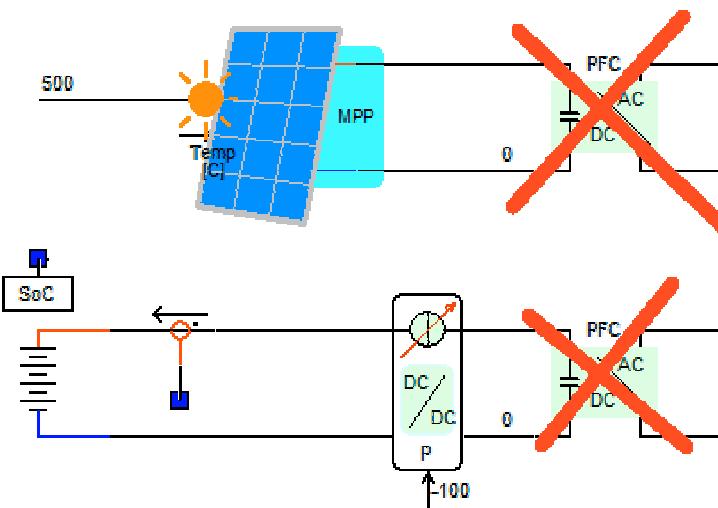


Combi-Cable in DC-netten

dr ir P.J.van Duijsen



Learning by Simulation

Simulation Research
The Netherlands





Welke Netten: MVDC

Caspoc
A simulation Experience

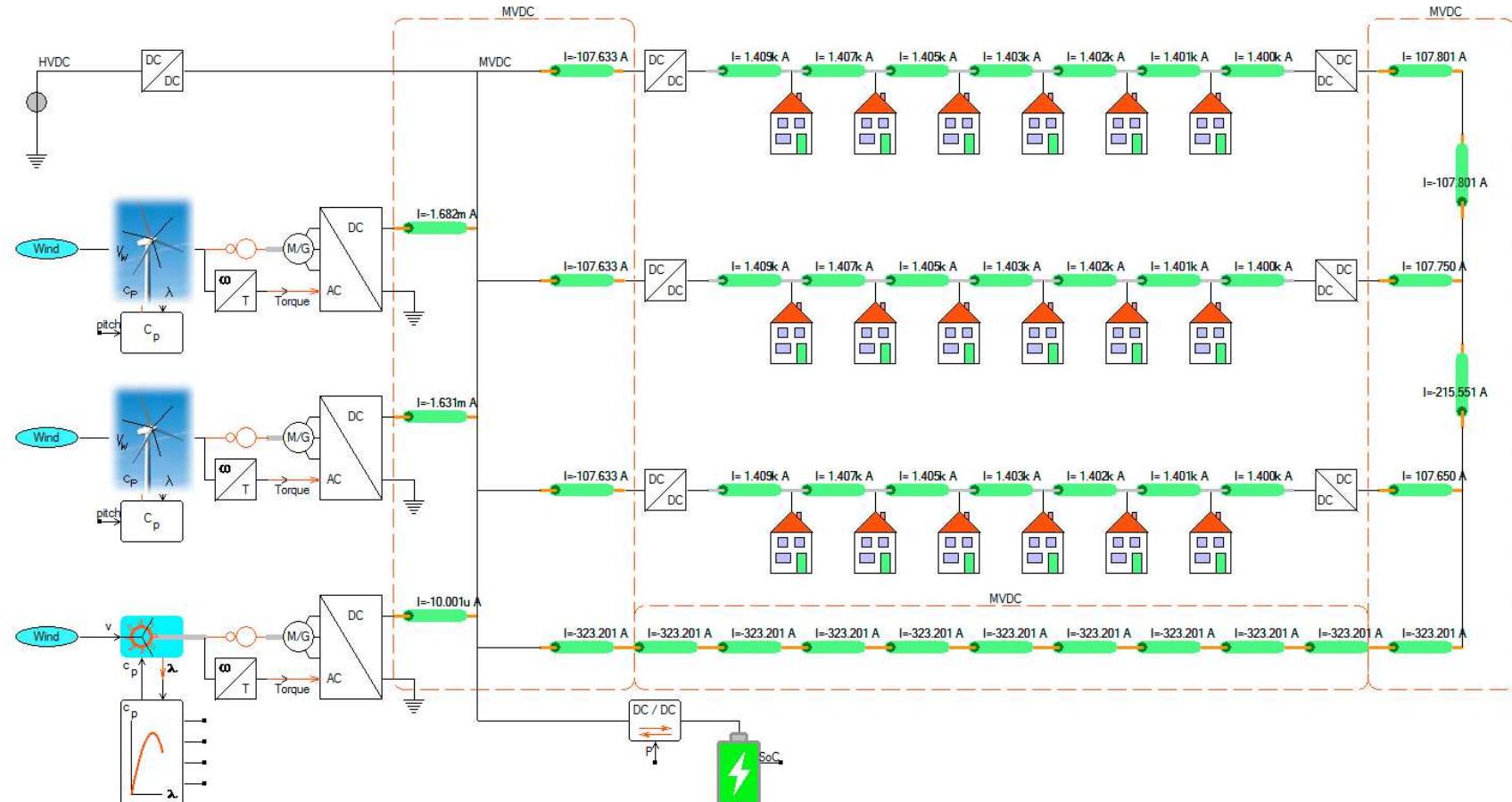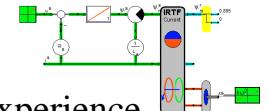



Welke Netten: LVDC

Caspoc
A simulation Experience

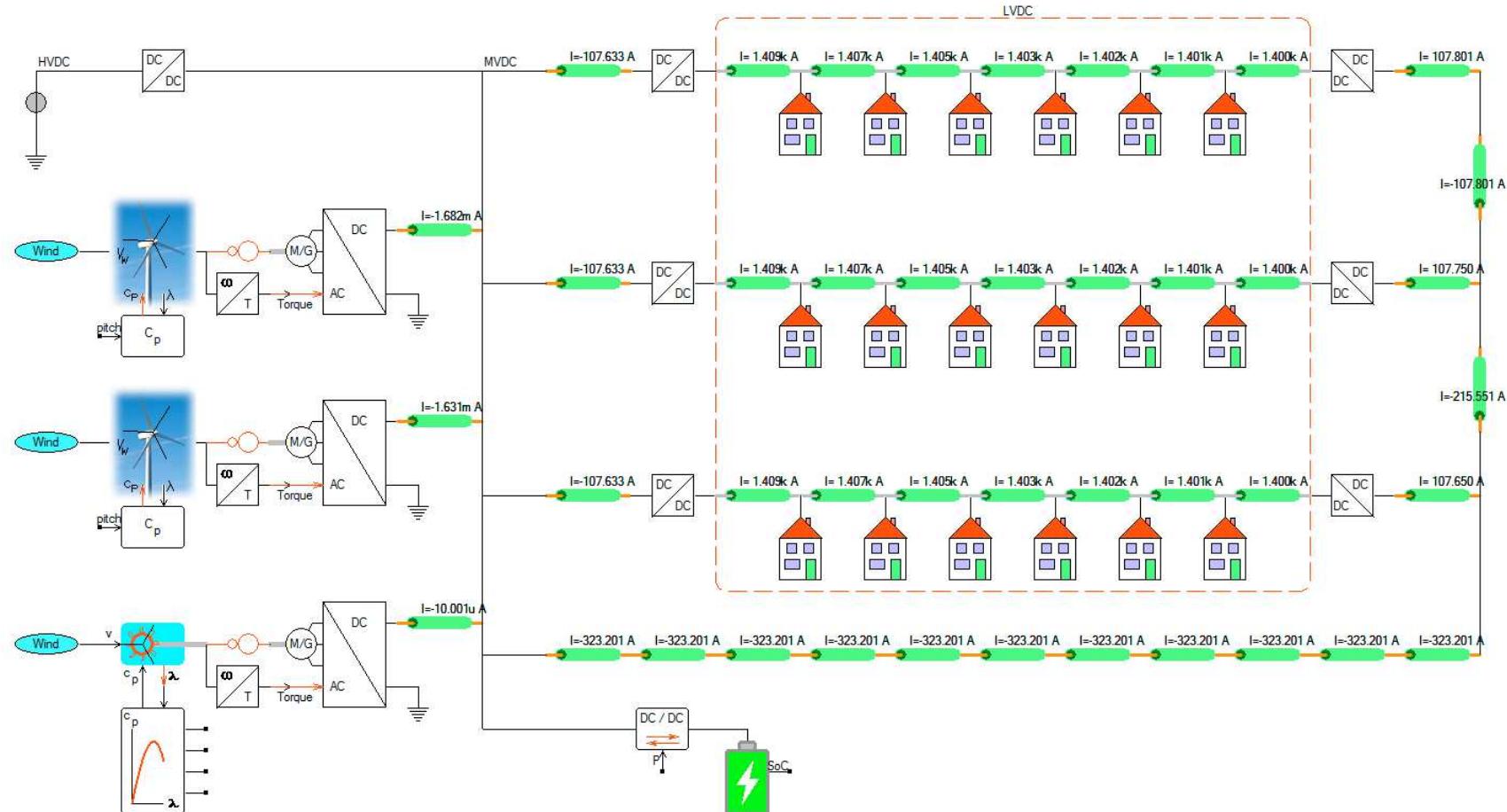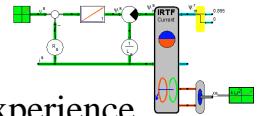


Welke Netten: Straatverlichting

Caspoc
A simulation Experience

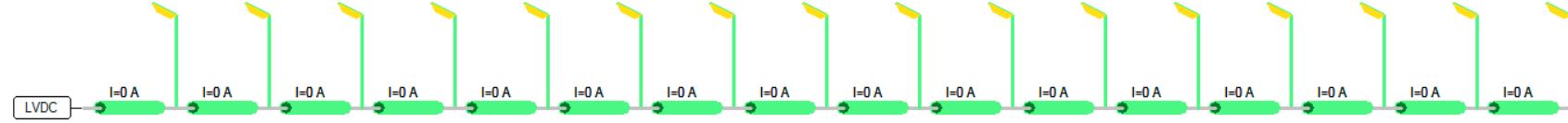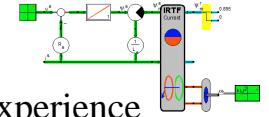

Cable Design tool

Caspoc
A simulation Experience

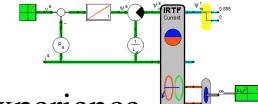

Caspoc Simulation & Animation X Product detail - TKF (Twentsch) X + caspoc.com/tools/powersystems/cable/sectorshaped/ Zoeken

Power Systems

POWER CABLES Sector-shaped Core

Tools > Power Systems > Power Cables > Sector-shaped Core [Copy link](#)

Cable geometry

Number of sectors	ns	4	[.]
Back radius	rb	16.4	[mm]
Insulation thickness (Leave 0 if ws and ds are specified)	t	1.8	[mm]
Sector depth	ds	12.7	[mm]
Sector width	ws	15.9	[mm]
Corner radius reducing depth	rcd	3	[mm]
Corner radius reducing width	rcw	3.5	[mm]
Sheath diameter	dsh	47.5	[mm]
Sheath wire diameter	dshw	1.15	[mm]
Number of sheath wires (Leave 0 to auto calc from heath diameter)	nsh	48	[.]
Cable diameter	dc	52.7	[mm]
Inner sheath isolation thickness	tis	1.4	[mm]


Auxiliary conductors

Cross section auxiliary conductor: [page 21](#)

Conductor Geometry

Calculate LCR

Caspoc
A simulation Experience



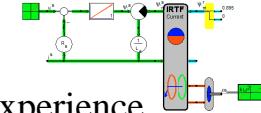


Nominal conductor diameter	d	13.4 [mm]
Nominal conductor cross section	$nccs$	140.935 [mm ²]
Geometric Mean Radius	GMR	5.6 [mm]
Geometric Mean Diameter	GMD	14.2 [mm]
Sector height	ds	12.6 [mm]
Sector width	ws	16.1 [mm]
Conductor Resistance		
Resistance copper wire	R_{CU}	126.5 [mΩ/km]
Resistance Aluminium wire	R_{AL}	200.2 [mΩ/km]
Conductor Inductance		
Self-Inductance	L_c	1037.6 [μH/km]
Mutual-Inductance	L_{mc}	851.3 [μH/km]
Mutual-Inductance diagonal	L_{m2c}	781.8 [μH/km]
Cable-Inductance(Given in datasheet)	L_{cable}	186.3 [μH/km]
Impedance	Z_c	58.516 [mΩ/km]
Conductor Capacitance		
Capacitance conductor-conductor	C_m	97.4 [nF/km]
Capacitance conductor-sheath	C_o	150.2 [nF/km]
Effective Capacity to Neutral(Given in datasheet)	C_{ist}	283 [nF/km]
Sheath Resistance		
Resistance sheath	R_{sheath}	357.7 [mΩ/km]
Sheath Inductance		
Self-Inductance	L_{sh}	932.8 [μH/km]
Mutual-Inductance Conductor-Sheath	L_{msh}	748 [μH/km]
Auxiliary Conductor		
Resistance copper wire	R_{aux-CU}	2972.5 [mΩ/km]
Self-Inductance auxiliary	L_{aux}	1366.8 [μH/km]
Mutual-Inductance auxiliary-core	L_{maux}	887.5 [μH/km]
Mutual-Inductance aux-aux	M_{aux}	138.6 [μH/km]
Aux-core Capacitance	$C_{aux-core}$	66.118 [nF/km]
Aux-sheath Capacitance	$C_{aux-sheath}$	78.518 [nF/km]
Coupling factors		
Coupling Core-Core	k_{cc}	0.82
Coupling Core-Core diagonal	k_{ccd}	0.754

Inductance

Caspoc



A simulation Experience

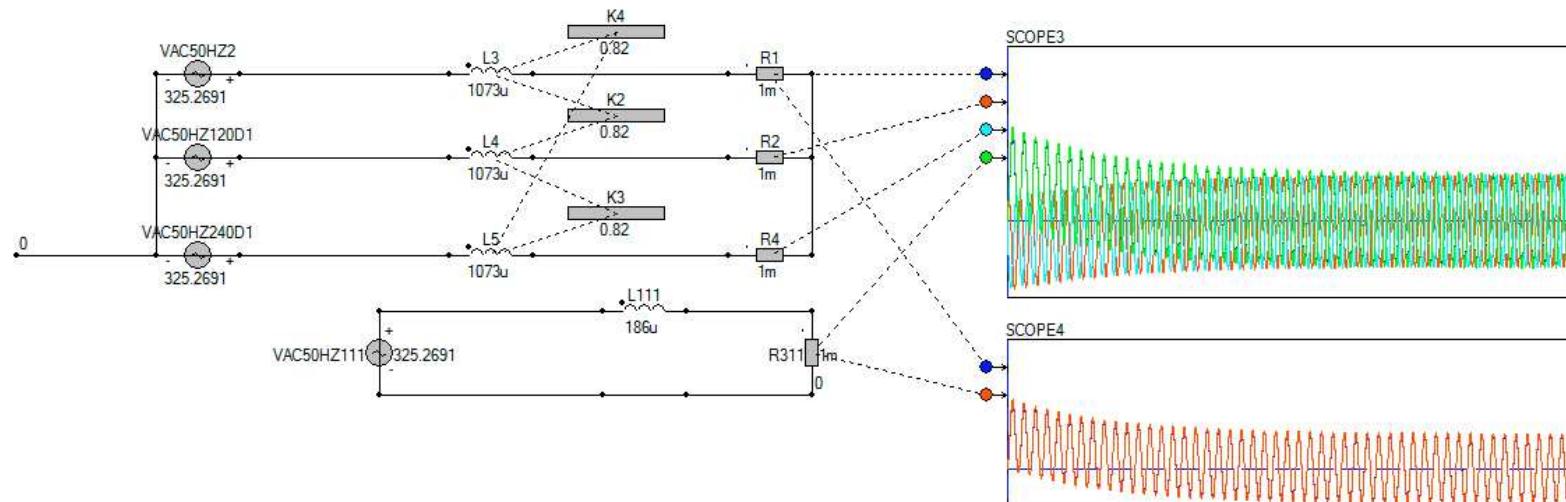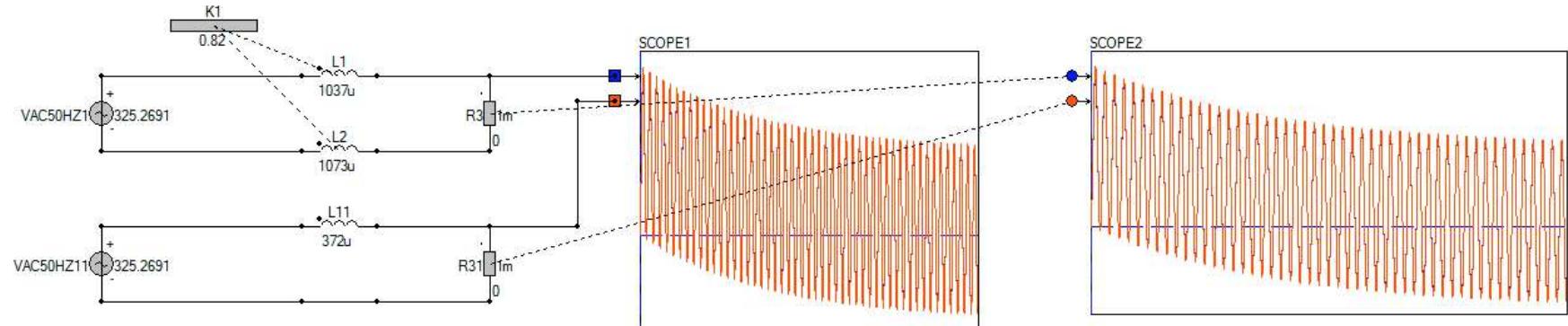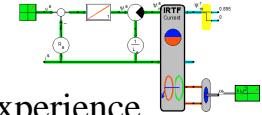

Capacitance

Caspoc

A simulation Experience

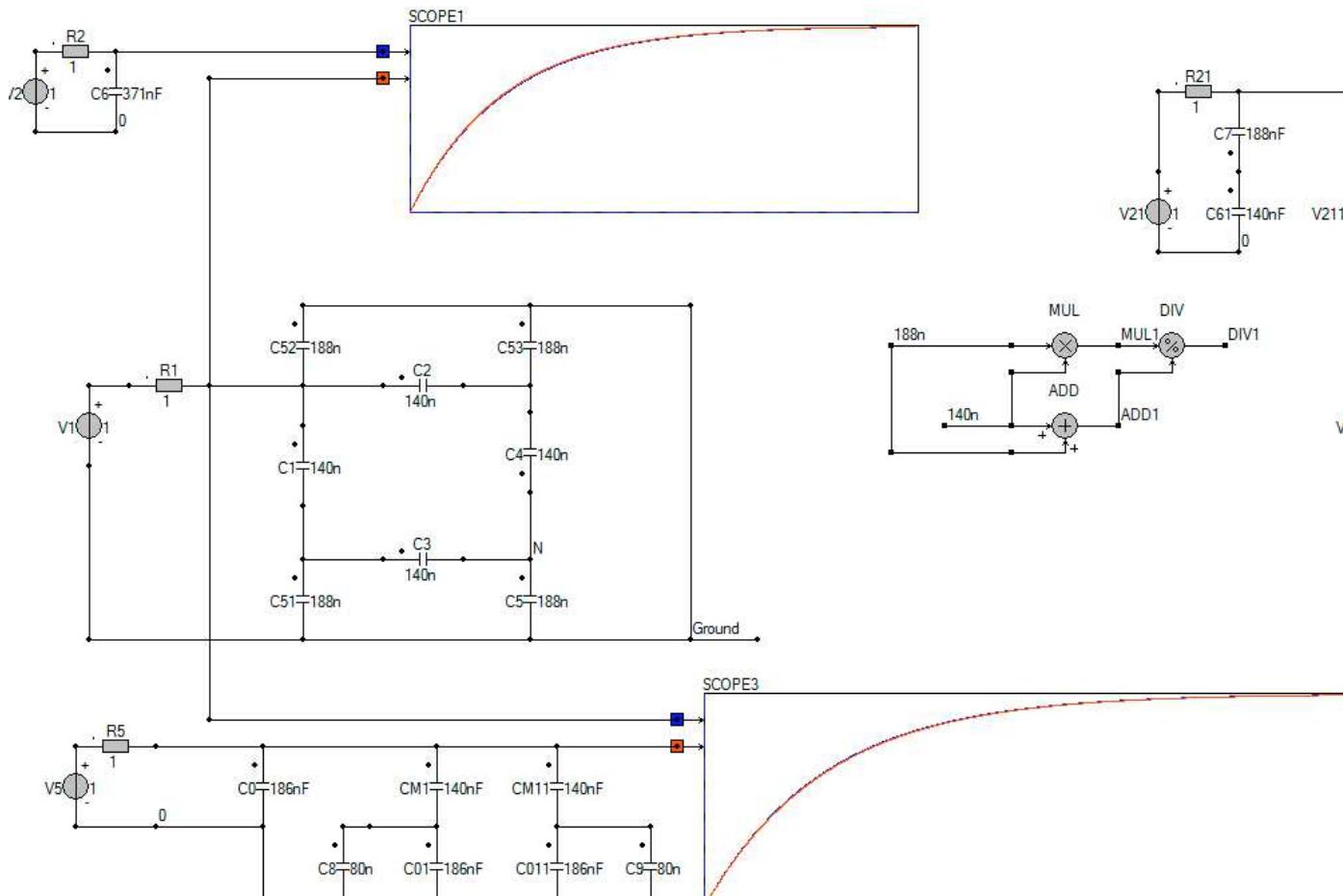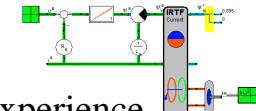



NOTE1

C0 core naar sheath
 Cm//Cx core naar naastgelegen core naar sheath
 waarbij Cx = C0 + Cm//C0 capaciteit van de daarnaast gelegen core naar sheath

Simulation

Caspoc



A simulation Experience

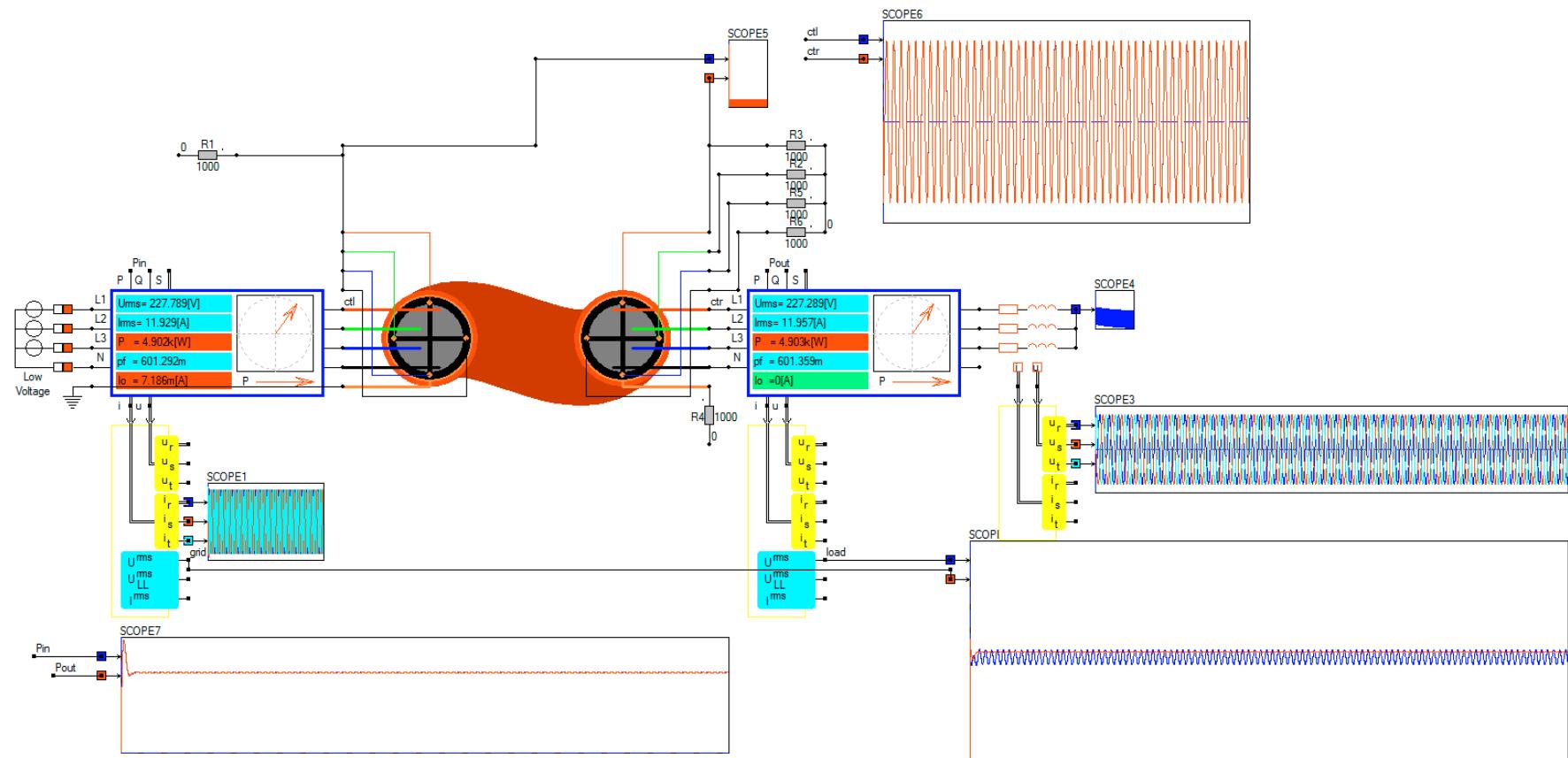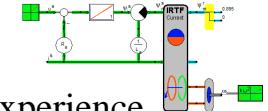

Change load from 5kw to 30kw

Caspoc



A simulation Experience

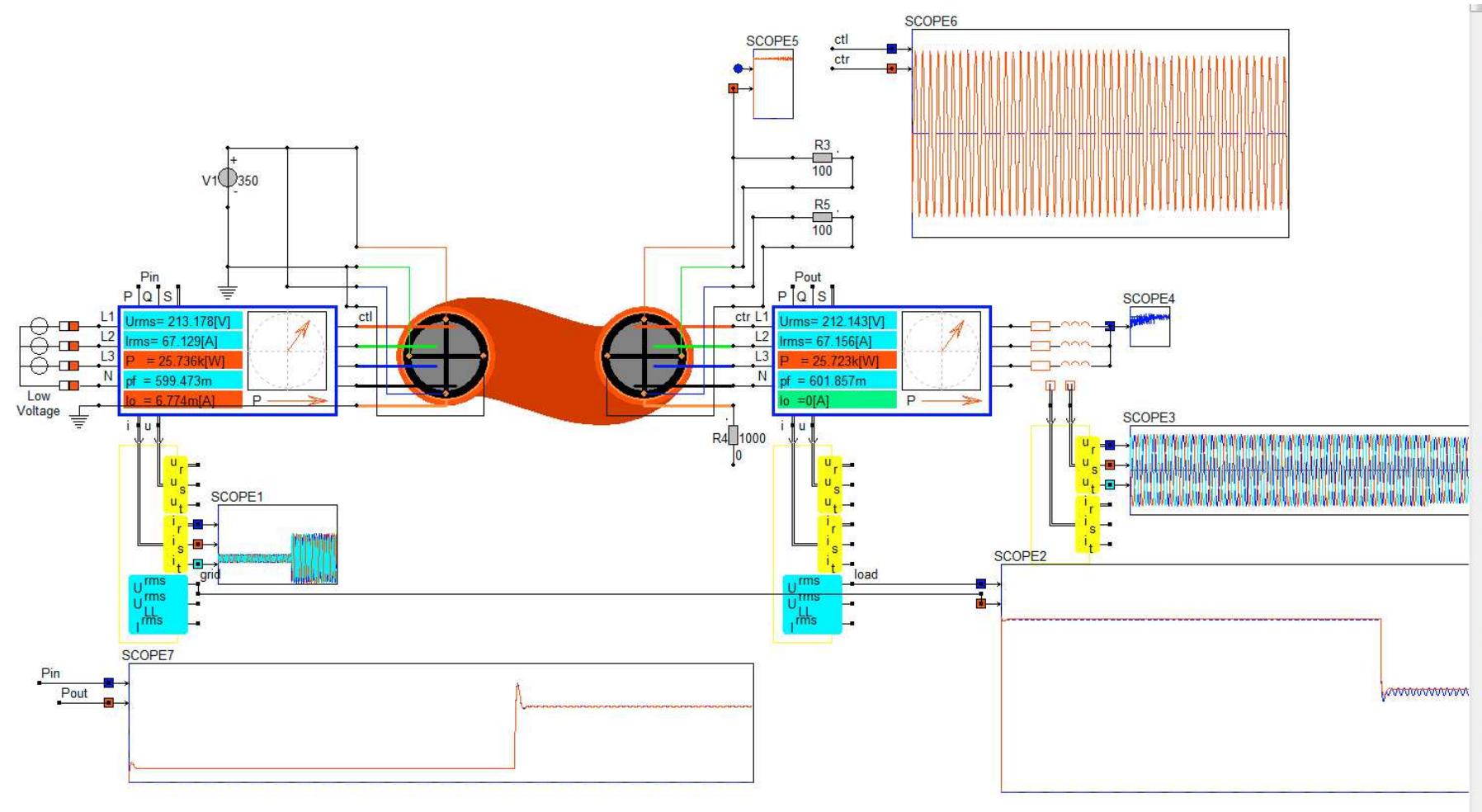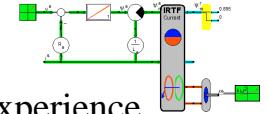

- More ripple on virtual neutral
- Higher ripple voltage on the auxilairy cores

Ripple on RMS input/output voltage



Caspoc
A simulation Experience

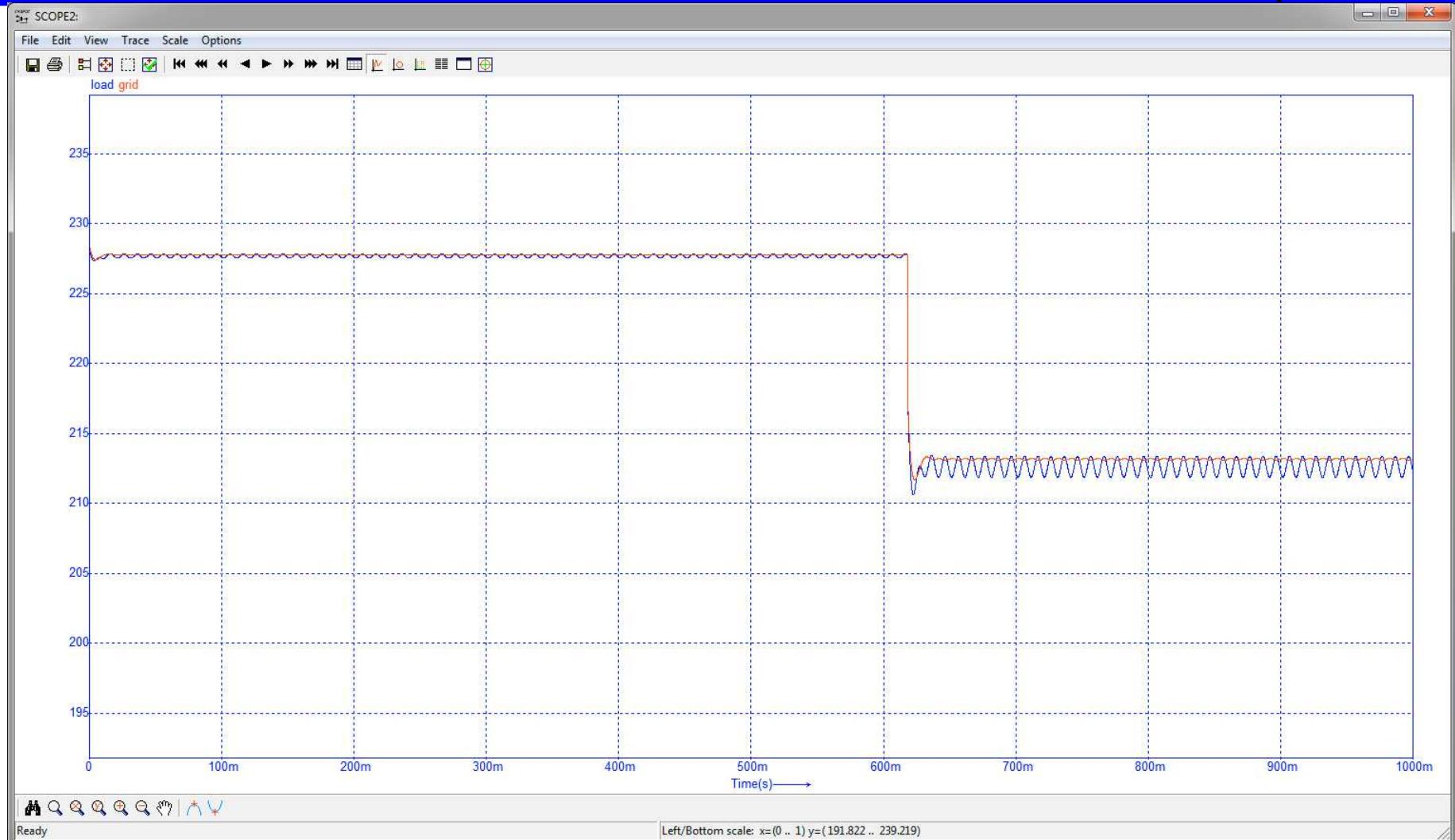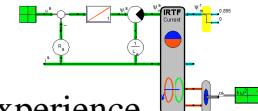

- RMS input/output voltage



Ripple on Auxilairy core

Caspoc
A simulation Experience

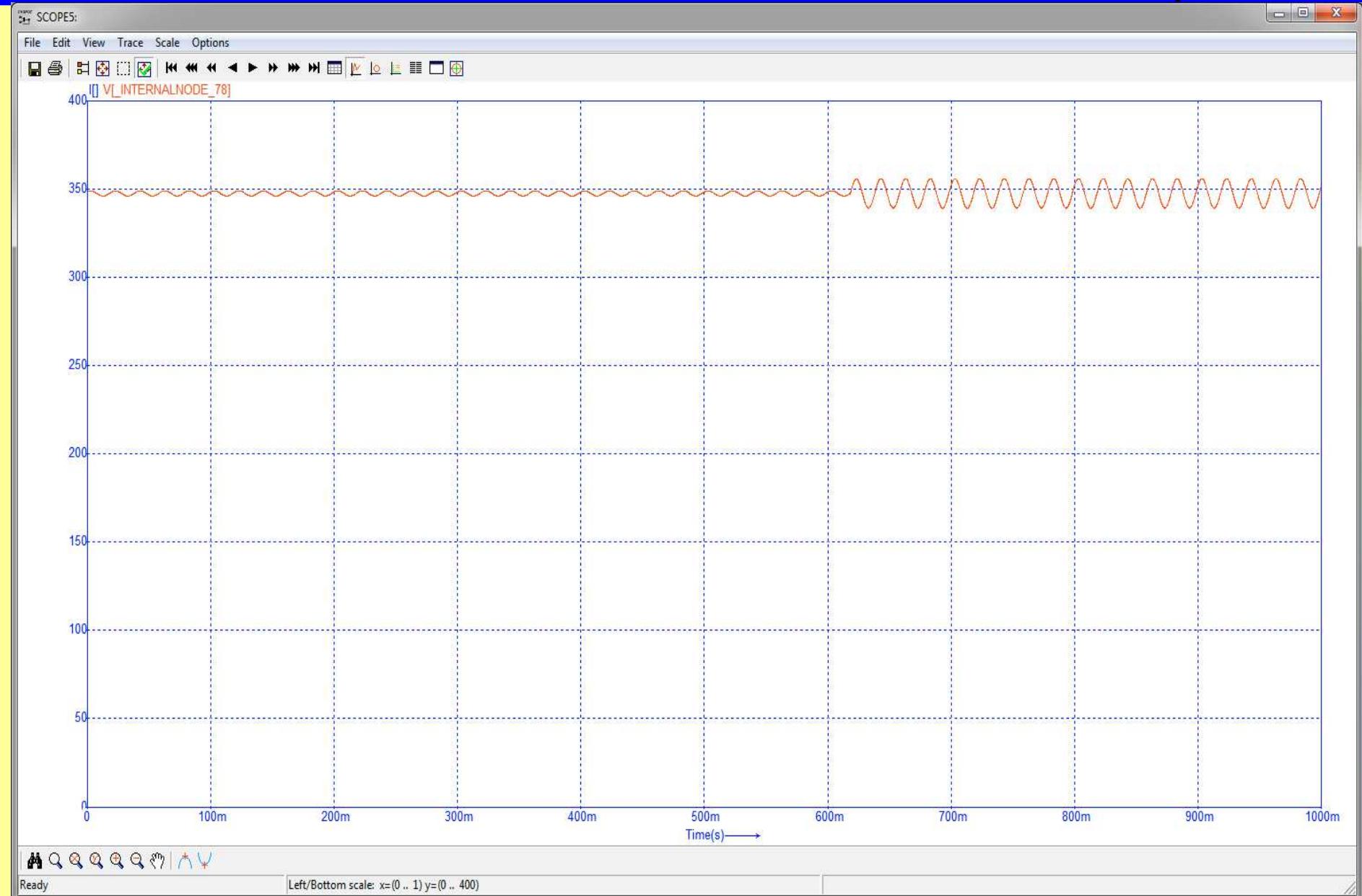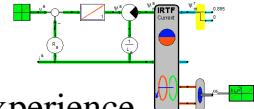



Change auxilairy core connection

Caspoc
A simulation Experience

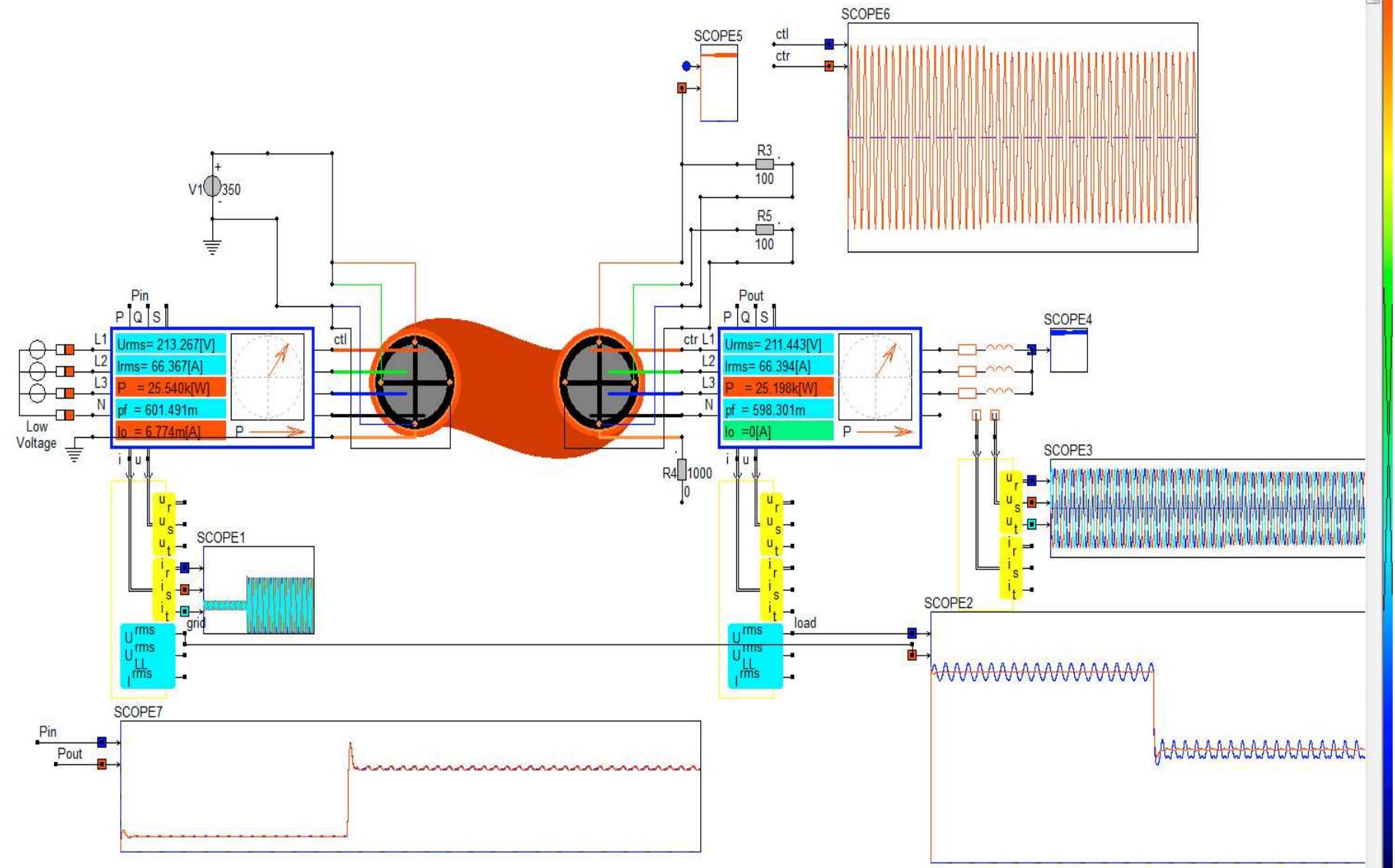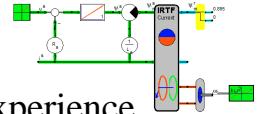



RMS input/output voltage

Caspoc
A simulation Experience

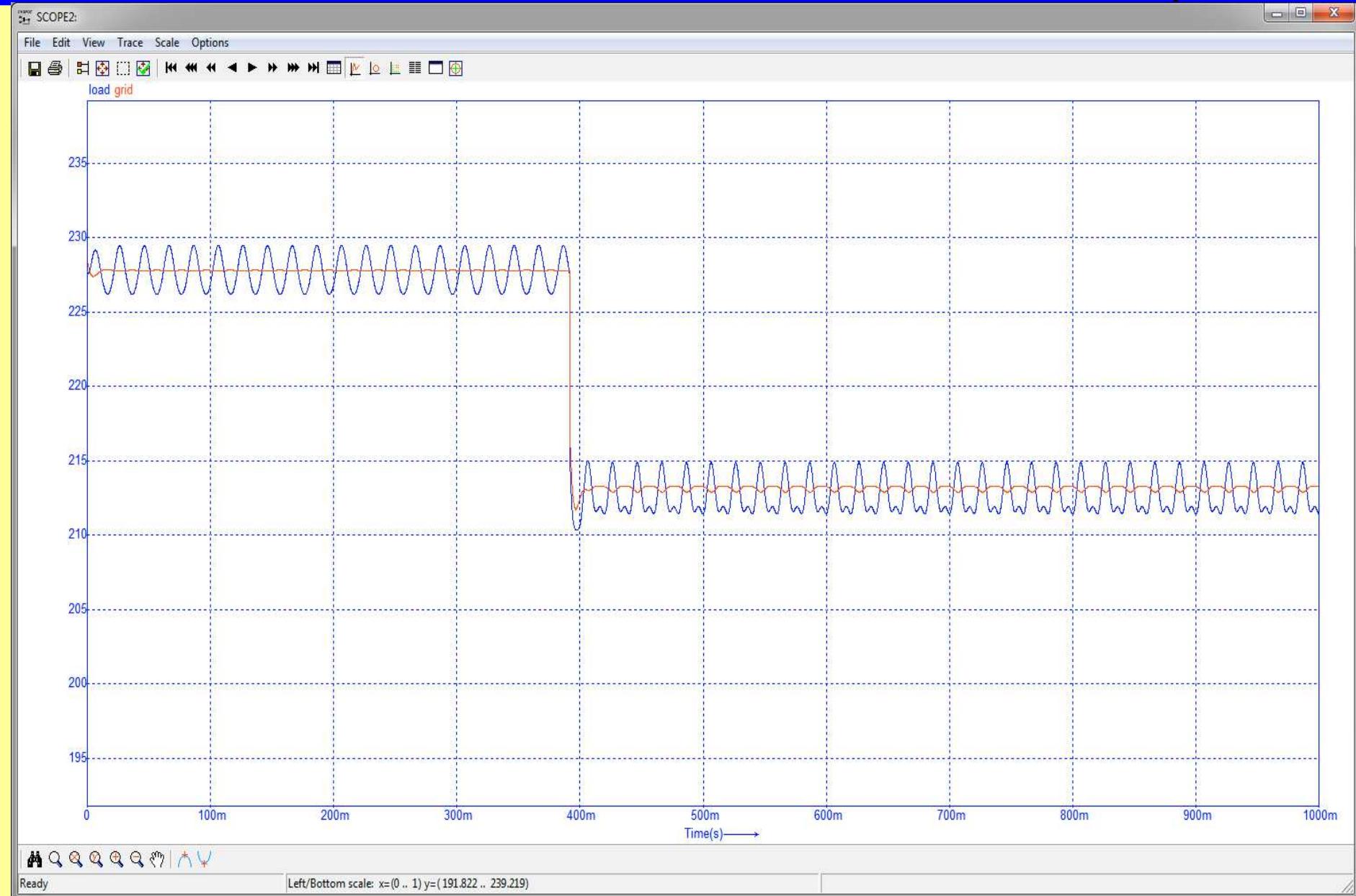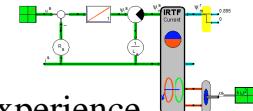



Voltage Auxilairy core


Caspoc
A simulation Experience

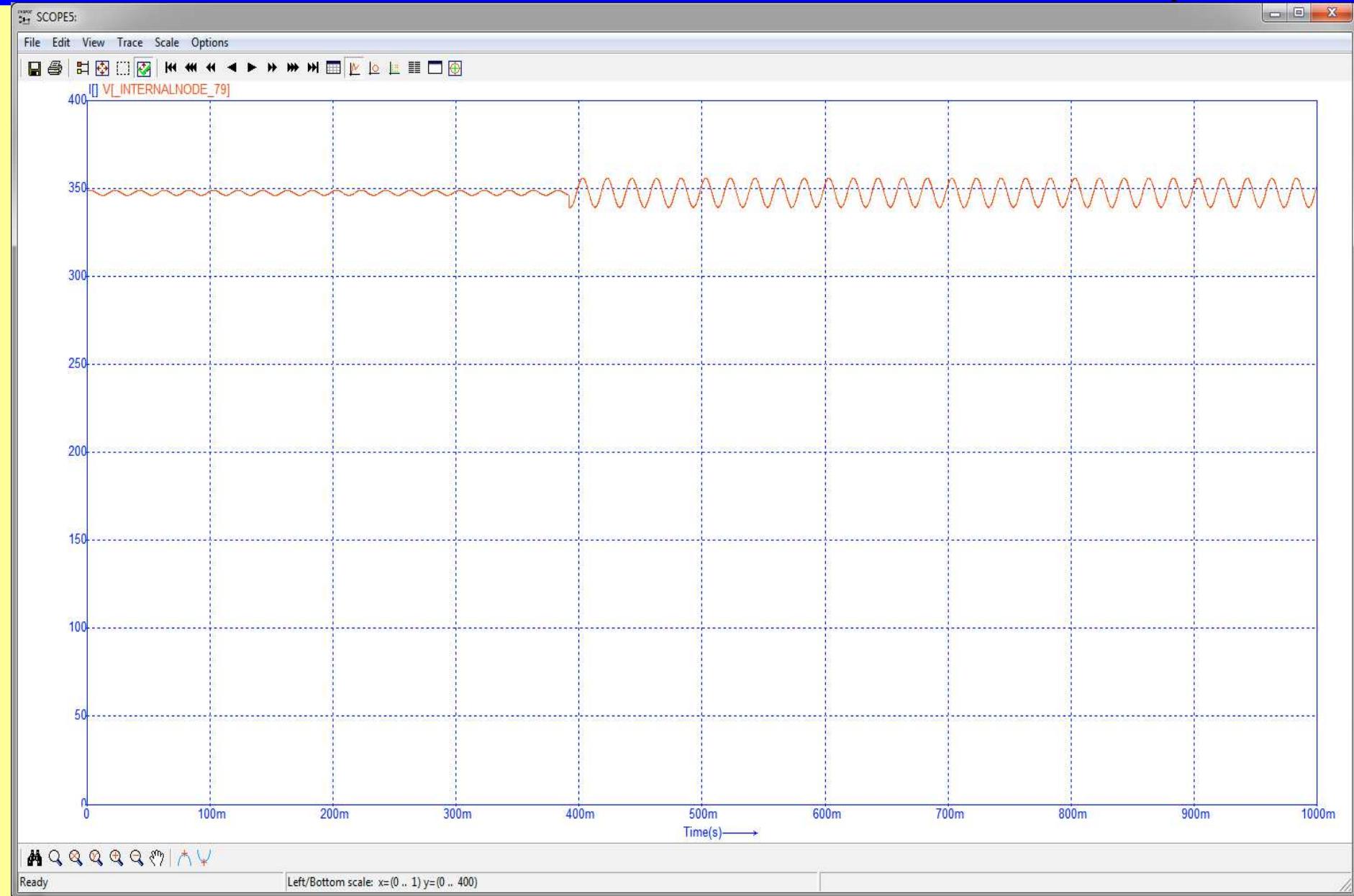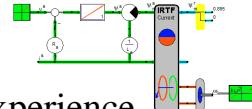

Voltage virtual neutral load

Caspoc
A simulation Experience

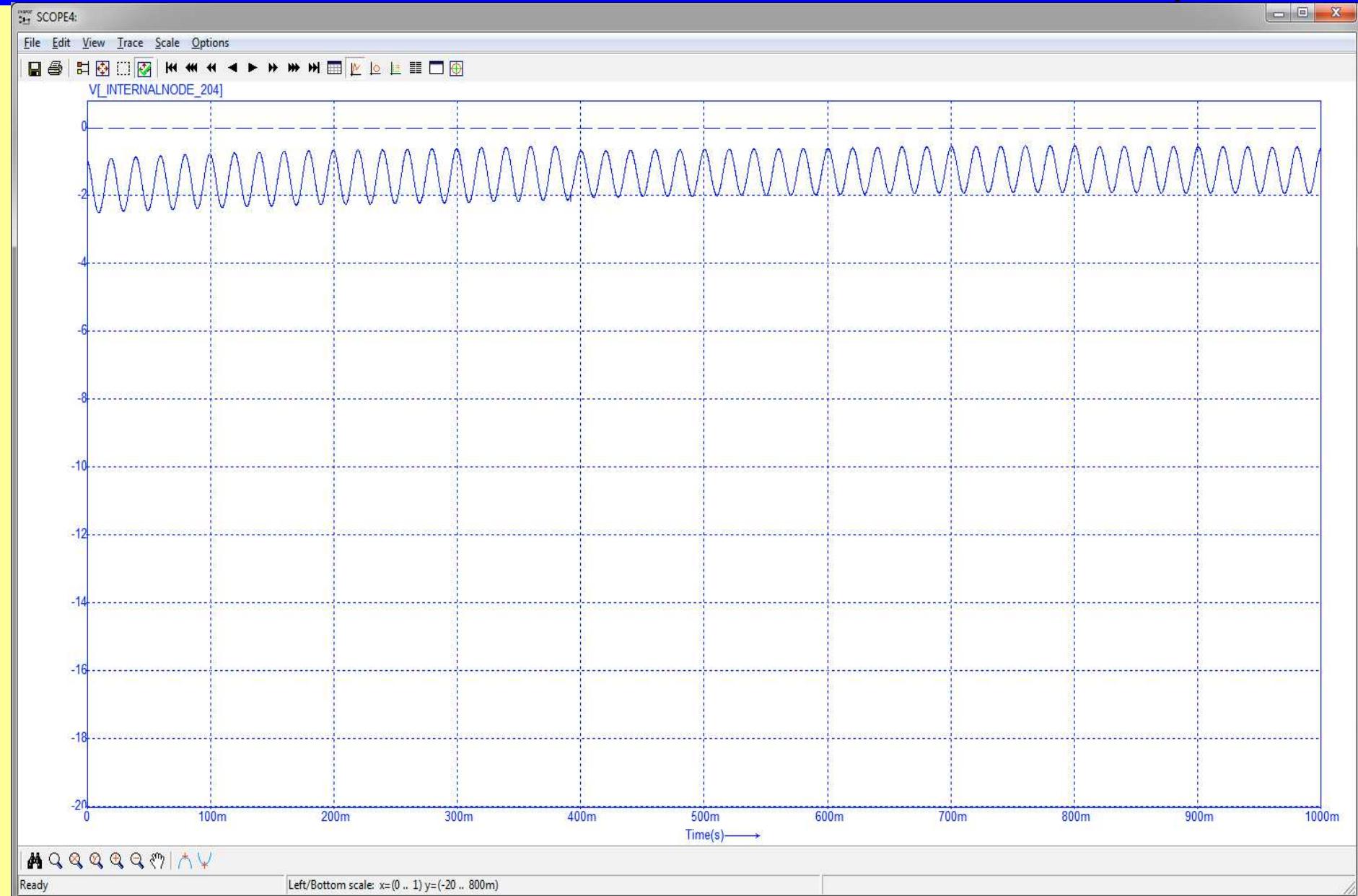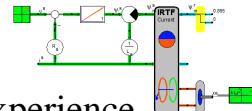

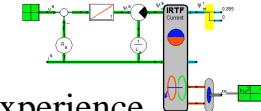

- Vragen?

